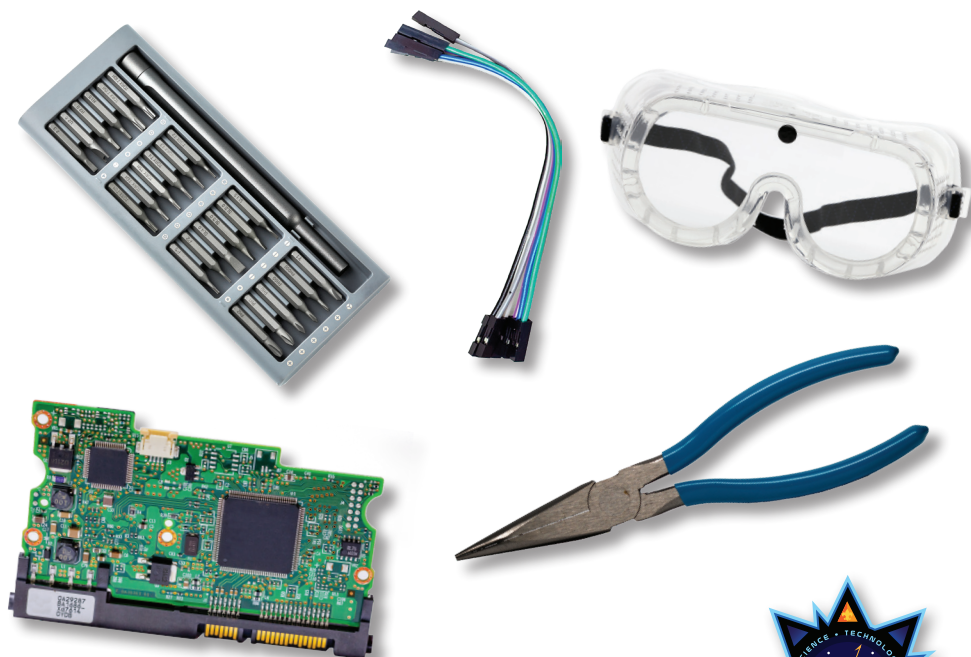


# MERIT BADGE SERIES



# ELECTRONICS



SCOUTING AMERICA  
MERIT BADGE SERIES

# ELECTRONICS



*"Enhancing our youths' competitive edge through merit badges"*

Scouting  America

# Note to the Counselor


For requirement 4, with the Scout's parent or guardian's approval and your acceptance, find an electronic kit in an area of interest to the Scout. It should be easy to order, build, and demonstrate.

Look for kits that use high-quality, durable components that are safe for youth. Check for certifications or endorsements from educational organizations. The kit should have a mix of various types of components and should require the Scout to solder 15 or more connections in the kit assembly. One kit per youth. Before building the kit, the Scout will need to find or create the schematic of the project and explain the function of all of its parts. Then the Scout can build the components and demonstrate its operation.
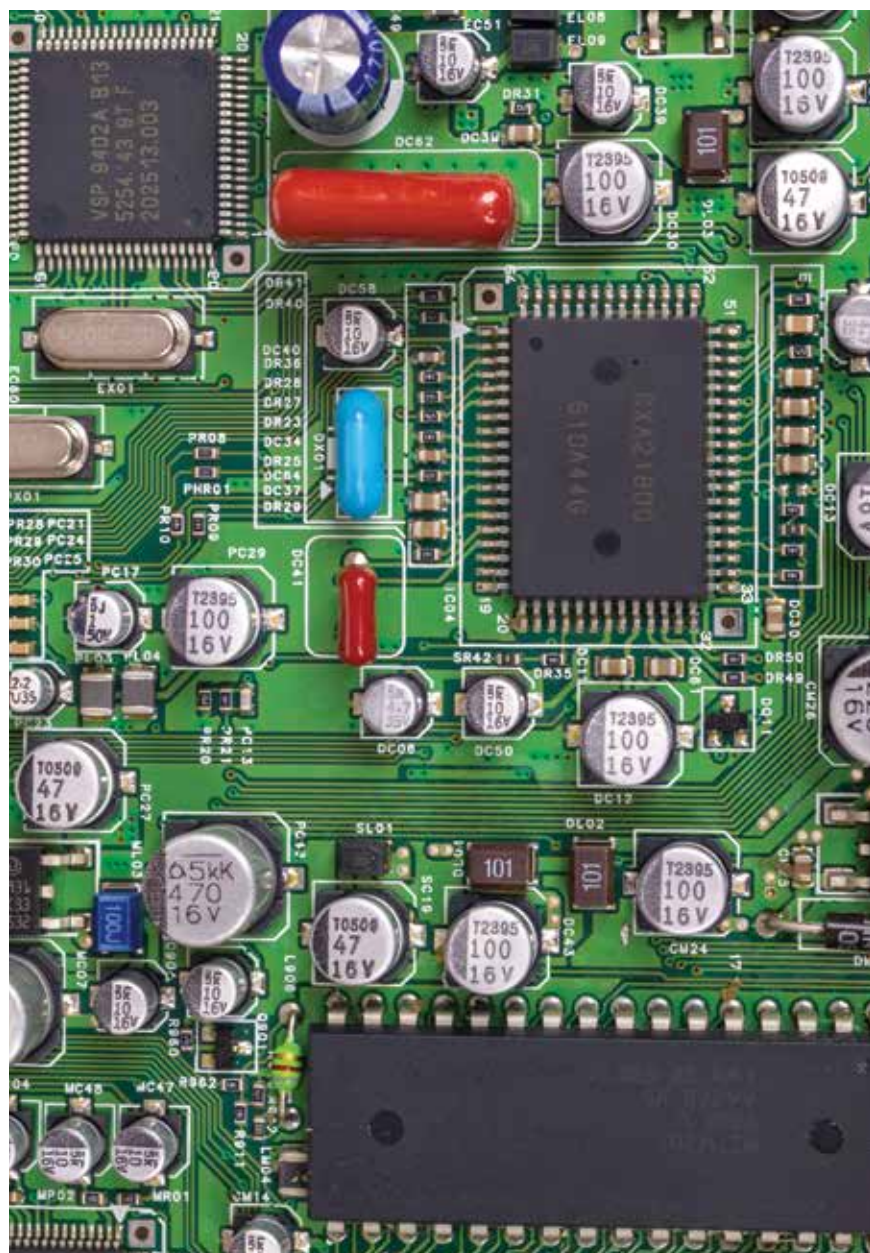
## Requirements


*Scouts should go to [www.scouting.org/merit-badges/Electronics](http://www.scouting.org/merit-badges/Electronics) or check Scoutbook for the latest requirements.*





## Contents

|                                      |    |
|--------------------------------------|----|
| History and Introduction . . . . .   | 7  |
| Tools for Electronics Work . . . . . | 11 |
| Basic Electronics Theory . . . . .   | 15 |
| Schematic Diagrams . . . . .         | 29 |
| Soldering. . . . .                   | 43 |
| Control Devices . . . . .            | 53 |
| Digital Electronics . . . . .        | 59 |
| Audio . . . . .                      | 69 |
| Electronic Test Equipment . . . . .  | 75 |
| Careers in Electronics . . . . .     | 83 |
| Electronics Resources. . . . .       | 86 |

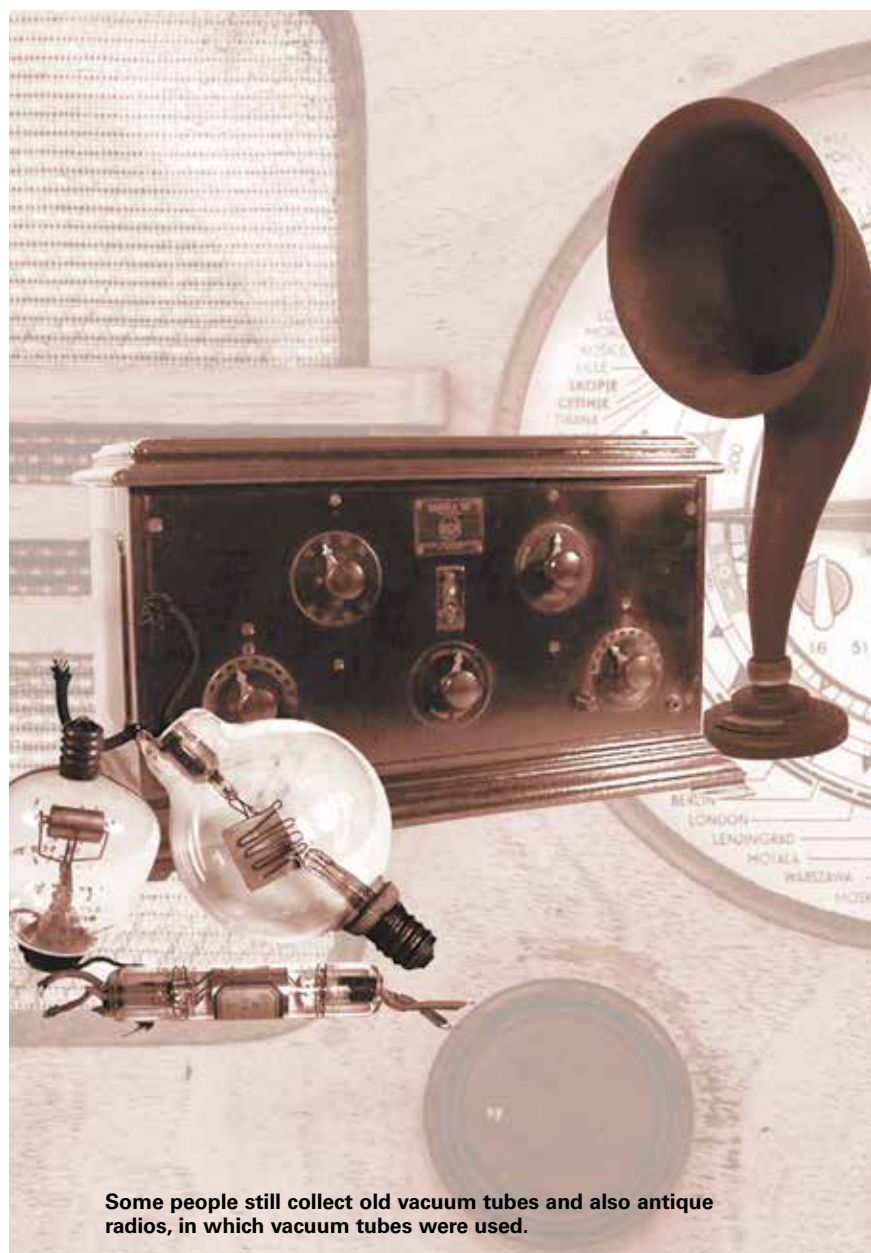

**Some people still collect old vacuum tubes and also antique radios, in which vacuum tubes were used.**

# History and Introduction

*Electronics* is the science that controls the behavior of electrons so that some type of useful function is performed. (Electrons will be explained more fully later in this book.) Today, electronics is a fast-changing and exciting field.

The rapid growth of electronics started in the early 20th century when vacuum tubes were introduced and used to manipulate electronic signals. This was something that could not be done with the telegraph and telephone circuits or the high-voltage transmitters of those days. Vacuum tubes allowed weak radio and powerful signals to be *amplified*, or to be made louder or stronger, and be sent on powerful waves.

Vacuum tubes were an important breakthrough in electronics, but they had their limitations. For example, early computers using vacuum tubes were so large that one computer would fill an entire room. These computers had minimal processing power because, for one reason, the tubes needed a lot of power to function.

Electronics changed even more dramatically in 1948 when the *transistor*, a small, low-powered, solid-state electronic device, was invented. Transistors are smaller than vacuum tubes, require less power to function, and are more reliable. The development of the integrated circuit, or IC, advanced this technology further. ICs can contain tens of thousands of tiny transistors built onto a small piece of conducting material. This allows for the construction and production of complex electronic circuits, which are more efficient than tubes in processing electronic signals. ICs are used in many products

today, including computers, audio equipment, cell phones, appliances, and automobiles.

## How to Earn the Electronics Merit Badge

The first step in earning your Electronics merit badge is to discuss the requirements with your merit badge counselor.

To fulfill requirement 1, learn about the precautions you should take when using, building, altering, or repairing electronic devices. Many electronic *components* (parts) could be

### Tips for Repairing Electronic Devices



1. Be sure to turn off and unplug the power before operating on any electronic circuit.
2. Always wear safety goggles when working with electronic devices, especially when soldering.
3. Be careful about *electrostatic discharge*—that “zap” you feel after you run across a carpet in socks and then touch metal. This can be a big problem in your electronics work. It can actually set materials on fire and damage electronic components. Before handling components, touch a piece of metal to discharge any static electricity.
4. Don’t force a component into anything you are working with, and don’t overtighten anything.
5. Be careful when you are working with wires. Bending a wire too often or tightening one too tightly could cause it to break.
6. When inserting plugs and sockets, ease them in and out. Never force them. Be aware that some components must be installed a certain way.
7. Be careful when using tools such as pliers and cutters so that you don’t nick any wires or cut your fingers.
8. When bending component leads, don’t bend them too closely to the body of the component because the component will be strained.

damaged if mishandled. Here are some basic safety precautions; there are more safety suggestions later in this pamphlet. As you read this pamphlet and work on the requirements, pay attention to safety and see whether you can add to this list.

For requirement 2, study the chapter called “Schematic Diagrams.” You may choose a schematic diagram from this pamphlet, then copy it carefully with a pencil. Your drawing must show resistors, capacitors, and transistors or integrated circuits. Use the correct symbols for these components, label all parts, and be prepared to tell the purpose of each component. Show your drawing to your counselor and tell what you have learned.

For requirement 3, learn how to solder and then practice soldering and desoldering wires. When you think you are ready, show your soldering skills to your counselor. Be prepared to discuss soldering precautions, printed circuit boards, and possible heat damage to components when using a soldering iron.

Requirement 4 is demanding but fun because you will actually build a working electronics circuit. Choose your project carefully. Make sure that all the required parts are available at an electronics parts store, from a catalogue, or over the internet (only with your parent or guardian’s permission). Also consider what tools you will need. You can choose a project other than those in this pamphlet, but check with your counselor first to make sure that the project is suitable. After you are done with the project, show it to your counselor and explain how it works.

For requirement 4 you will also learn the basic principles of digital techniques, how you can use electronics for control purposes, and about audio applications. Learn the binary system so that you know how to change decimal numbers into binary numbers and binary into decimal.

For requirement 5, you will need to solve a simple problem using Ohm’s law. You also should be able to discuss test equipment, the different types, and what they’re used for.

For the final requirement, study three career opportunities in electronics that interest you. Discuss with your counselor the education and training needed for each.



# Tools for Electronics Work

The basic tools you will need for most of your electronics work are shown here. You can probably find some around your home and get others at an electronics parts store.

## Some Basic Tools



**Slotted (flat-bladed) screwdriver**



**Phillips screwdriver**



**Nut driver**



**Cutting pliers**, which cut either flush or diagonally, cut wires and trim soldered leads.



**Long-nosed pliers** are used to bend leads on components and hold parts while you solder.



**Tweezers**, straight or curved, are used for handling small components.




**This multipurpose electrical tool removes insulation from wires before soldering. You also can use a hobby knife for stripping wires and trimming.**

Electronic parts are called *components*, which comes from the word meaning *to put together*. An electronic *circuit* is composed of several interconnected components. The *leads* on a component are electrical conductors, such as wires, that connect to an electrical device.

For most projects, you can use any small-diameter solid or stranded hookup wire. Some projects might also require very small wire. A magnifier or magnifying work lamp is recommended for examining the circuit board to check solder connections. Most electronics parts stores have a selection of perforated circuit boards made specially for wiring electronics projects. Many come with small clips for mounting parts. These boards are ideal for building simple circuits.

You also will need an electric soldering iron, which you can buy at a hobby, electronics parts, or hardware store. The soldering iron in a beginner's tool kit should be a 15- to 40-watt iron with a fine chisel tip. Use 60/40 rosin-core solder (60 percent tin, 40 percent lead) that is marked for "electronic use." Never use acid core solder. Most of the solder you will need will have a diameter of 0.03 inch. You also should have a solder wick for desoldering a connection if you make a mistake or want to remove a component.

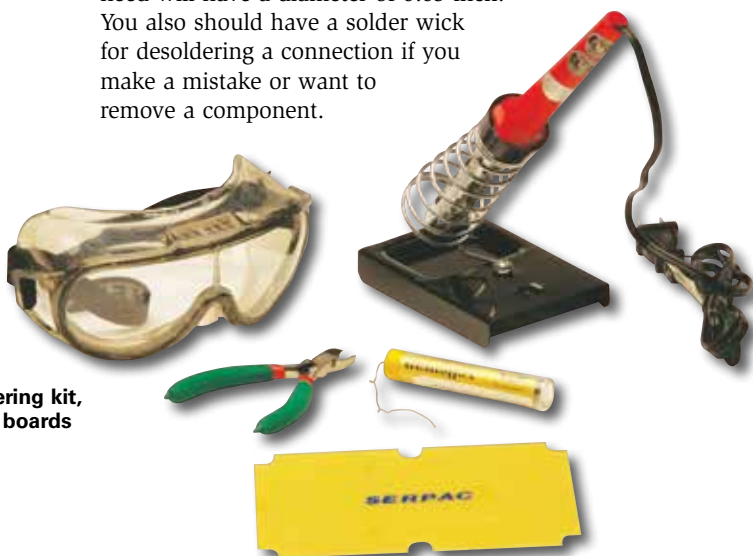

**Basic soldering kit, perforated boards**

Use a workbench for your project if you have one. If not, you can use a kitchen table, desk, or sturdy card table. You will need to have good light and ventilation and access to power outlets. You also will need a few small boxes, trays, or jars to hold parts.

---

Get your  
counselor's  
approval before  
you start  
your project.

---

## Buying Parts

Most electronics parts stores will have the components you will need for your project. If you do a project from scratch, you will have to buy the parts separately. While you also can buy a complete project as a kit, many electronics kits found in retail stores are not soldering kits, and building a project from scratch is challenging and rewarding. Scratch projects can be inexpensive if you can scrounge for most of the parts.

However, a kit has a number of advantages. All the necessary assembly instructions and parts are supplied, including wire and solder. Special parts, such as printed circuit boards, come with the kit. In addition, fewer tools are required because all necessary holes are prepunched. Since the kit has been carefully tested, you know that the finished product will work. A complete kit generally costs less than buying the parts separately. Investigate doing a project both ways before you invest your money.



**Kit project**



# Basic Electronics Theory

Before you learn about electronic components, let's look at the theory behind electronics. Controlling electrons is the science of electronics. So, our study of electronics theory begins with the electron.

## Atoms and Electrons

To understand electrons, we must learn about the makeup of matter. All matter is composed of *atoms*, and an atom is composed of three elementary particles: *electrons*, *protons*, and *neutrons*. Negatively charged electrons revolve around the core (the *nucleus*) of the atom, which is composed of positively charged protons and neutral (not charged) neutrons.

Generally, a negatively charged electron is matched by a positively charged proton. For example, copper has 29 electrons revolving around a nucleus containing 29 protons. A basic law of nature controls electrical charges. This law simply stated is that *unlike charges attract and like charges repel*. This means a negative charge is drawn to a positive charge but pushes away from another negative charge. This is called *electrostatic force*.

Normally, the positively charged protons hold the negatively charged electrons in place. However, an electron sometimes breaks away from an atom because of an outside force, such as heat, light, magnetic fields, or chemical reactions.

Electrons have a negative charge. So if an object loses electrons, it becomes positively charged. If an object gains electrons, it then has a negative charge. A unit of electrical charge is called a *coulomb*.

Once freed, electrons can “float” among atoms. These *free electrons* are what is important in electronics. Devices such as resistors, capacitors, inductors, and transistors are used to control the behavior of these free electrons.

## Conductors and Insulators

*Conductors* act as a pathway for free electrons. Most metals are good conductors of electrons, so they can be used to “transport” electrons from one place to another. *Insulators* act as walls or barriers, preventing electrons from flowing where we do not want them to flow. Insulators, for example, are used on most electrical wires to protect us from electrical shock.

Copper, silver, and gold are popular conductors because they have a large number of free electrons. As an example of how to make the electrons flow, picture a length of copper wire with one end connected to the positive terminal of a battery and the other end connected to the negative terminal. The positive terminal attracts the negatively charged free electrons of the wire (remember: unlike charges attract) while at the same time the negative terminal repels the electrons. The result is a flow of electrons through the wire from the negative to the positive terminal. This flow is called an *electric current*.

An insulator works just the opposite. In some materials, such as plastics and glass, atoms hold their electrons tightly. These materials have very few free electrons. Therefore, if a length of insulator is connected to a battery the same way the copper wire was attached, no measurable current would flow.

## Current, Voltage, and Resistance

Here are some basic definitions of terms used in electronics.

- *Current* is the orderly movement of electrons through a conductor. Current is measured in *amperes*, or amps, or the rate at which electrons move past a given point. One ampere is the movement of about 6 billion billion electrons past that point in one second.
- *Voltage* is an electrical pressure that can cause current to flow. Voltage forces current to flow through a wire in much the same way that water pressure forces water to flow through a pipe. This electrical pressure can be caused with magnetism, chemicals, friction, light, or heat. The unit of voltage is the *volt*.
- The opposition to current flow is *resistance*. The resistance of a material is mainly determined by how many free electrons it has. If the material doesn't have many, it will have little or no current flow. The unit of resistance is the

A standard flashlight battery can produce 1.5 volts. A car battery produces about 12 volts. A light bulb in your home operates on 115 volts, while an electric stove requires about 220 volts.

*ohm*. One ohm is the amount of resistance that will allow 1 ampere of current to flow when the applied voltage is 1 volt.

## Frequency

Frequency, or cycles per second, uses the term hertz as its unit of measure. The electricity from electrical utilities is 60 Hertz AC and the voltage changes in a sine wave pattern.

## Know Your Units of Measure

- Electrical charge is measured in *coulombs*.
- Current is measured in *amperes*, or amps.
- Voltage is measured in *volts*.
- Resistance is measured in *ohms*.
- Electrical power is measured in *watts*.
- Capacitance is measured in *farads*.
- Frequency is measured in *hertz*.

## Ohm's Law

Ohm's law describes the basic relationships between current, voltage, and resistance. The formula for Ohm's law is:

$$\text{Voltage (volts)} = \text{Current (amperes)} \times \text{Resistance (ohms)}$$

To determine current, the formula would be:

$$\text{Current (amperes)} = \text{Voltage (volts)} \div \text{Resistance (ohms)}$$

If you know current and resistance, you can find out the voltage. For example, how much voltage is needed to force 2 amperes of current to flow through 10 ohms of resistance? Ohm's law tells us that we need to multiply our 2 amperes (current) by the 10 ohms (resistance) to arrive at the answer: 20 volts.

If you know voltage and resistance, you can figure out current (Voltage  $\div$  Resistance). Therefore, how much current will flow in a circuit having 5 ohms of resistance when 15 volts are applied?

$$15 \text{ volts} \div 5 \text{ ohms} = 3 \text{ amperes}$$

With these formulas, you can solve simple problems involving current, voltage, and resistance.

## Power

Another electrical quantity is power. Power is the rate at which work is done. The unit of electrical power is the *watt* and can be compared to the unit of mechanical power, called *horsepower*. One horsepower is equal to 746 watts. The formula for power is

$$\text{Power (watts)} = \text{Voltage (volts)} \times \text{Current (amperes)}$$

When this formula is applied, you can determine the amount of power used by a circuit if you know the voltage and current. For example, how much power is used by a 120-volt toaster that draws 5 amperes?

$$120 \text{ volts} \times 5 \text{ amperes} = 600 \text{ watts}$$

The power used by the toaster is 600 watts. This power is used, or dissipated, in the form of heat to toast the bread.

James Watt, a Scottish engineer and inventor in the 18th and early 19th centuries, actually tested horses hauling coal to help him arrive at the determination that 1 horsepower is the amount of power required to lift 33,000 pounds 1 foot in 1 minute. The watt is named after him.

## Current Delivery

Electrical signals are classified as either direct current (DC) or alternating current (AC). Direct current signals are at a constant voltage or at a constant polarity where AC signals typically follow a sine wave or other pattern and alternate between positive and negative voltages. If the AC signal follows a specific pattern, the number of times the pattern repeats

within one second is the signal's frequency. The electricity from electrical utilities is 60 Hertz AC and the voltage changes in a sine wave pattern.

## Resistance and Resistors

You have learned that when you apply a voltage to the ends of a conductor, it creates a current. Its strength depends on the applied voltage and the resistance of the conductor. The resistance of a conducting material depends on three factors:

1. The kind of material
2. The length of the material
3. The diameter or thickness of the material

Temperature also is a factor in resistance. In most materials, resistance is increased when the temperature rises and decreased if the temperature is colder. In most simple circuits, however, temperature is not critical and is often ignored. The *kind of material* is probably the most important factor in resistance.

Copper, for example, is a good conductor, while iron of a similar size has a higher resistance. Carbon has even a higher resistance than iron.

*The longer the conductor*, the higher the resistance will be. For instance, if the length of a copper wire is doubled, the resistance will be doubled. As an example, a 60-foot length of copper wire might have a resistance of 1 ohm. A same-sized copper wire that is 120 feet long would have a resistance of 2 ohms.

*Size is important*, too. A thick conductor will carry more current and offer less resistance than a thin one. Think again of water pipes. A large water pipe will allow more water to flow than a small one. When a current flows through a *resistor*, a component that limits or opposes the flow of a current, work is being done to move the electrons. This work produces heat and warms the resistor. Heat produced by an electric current is the basis for the operation of many electrical devices and appliances such as heaters, toasters, stoves, and soldering irons.

In a lightbulb, an electrical current causes a wire filament to become so hot that it glows to produce light. Only a fraction of the power that comes from the filament produces light. The rest generates heat, which is why incandescent bulbs are so inefficient. A resistor is designed to have a specific value of resistance, and resistors are available in a wide range of values. Standard power sizes are  $\frac{1}{4}$  watt,  $\frac{1}{2}$  watt, 1 watt,

and 2 watts. These values indicate the maximum recommended power that the resistor can dissipate. The higher the power rating, the larger the resistor.

## Capacitors and Capacitance

A *capacitor* is a device for storing electrons, or an electrical charge, that can be released at a later time. Imagine two sheets of aluminum foil (conducting plates) that are separated by a sheet of waxed paper (an insulator). If you connect a battery to the two aluminum sheets, electrons will flow from the sheet that is connected to the positive terminal of the battery. Simultaneously, the same number of electrons will flow from the negative terminal of the battery to the other aluminum sheet. The number of electrons that are transferred makes the voltage between the aluminum sheets exactly that of the connected battery. If the battery is removed, the aluminum sheets will remain in their charged state. If there is no leakage through the waxed paper, the sheets will remain charged indefinitely.

Any two conducting plates separated by an insulator make up a capacitor. A capacitor can consist of many conducting plates with insulating separators. Alternate plates would be connected to form interleaved stacks.

The higher the voltage, the greater will be the amount of charge that is transferred from one plate to the other. The ratio of charge to voltage is defined as the *capacitance* of the capacitor. Or you could also say that the “electrical size” of a capacitor is its capacitance, which is the amount of electric charge it can hold. The unit of capacitance is the *farad*. However, this unit is too large for most practical capacitors, so capacitors are manufactured to measure millionths of a farad (microfarads) and trillionths of a farad (picofarads, which are micro-microfarads).

The insulators that separate conducting plates in a capacitor can be made of several materials, including ceramic materials, mica, certain types of paper, air, and oxide (a compound containing oxygen). A popular capacitor has been the electrolytic capacitor. In this capacitor, the insulator is an extremely thin oxide layer. The leads of electrolytic capacitors are marked positive and negative. These indicate how the capacitor must be connected for proper operation.


## Electron Tubes

The electron tube made the science of electronics possible. Although it largely has been replaced by transistors, it still has special uses. Tubes for high power are still used today in lasers, radars, strobe lights, and special-use vacuum tubes. Many high-end stereo collectors still prefer the sound of a tube amplifier over that of a transistor amplifier.
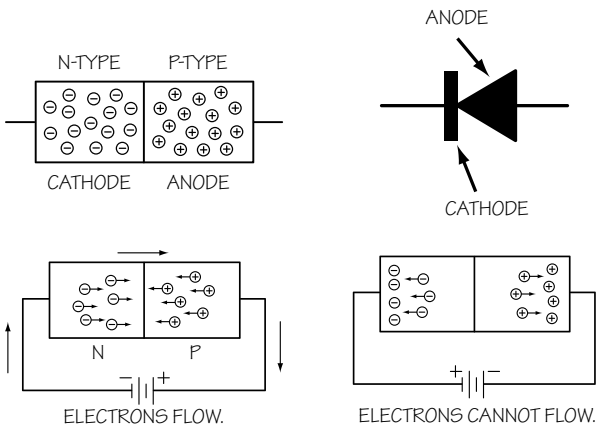
## Semiconductors

The word *semiconductor* is used to name a wide variety of electronic devices. Made of solid or liquid material, semiconductors generally are able to conduct electricity more easily than an insulator, but not as easily as a metal.

The **semiconductor diode** performs the same basic function as the electron-tube diode. It allows current to flow in one direction, but not the other. This diode consists of two different types of silicon crystals. An impurity (some type of substance) can be added to one area of the silicon to control the silicon's conductivity. The silicon is said to have been "doped" when it has been treated with atoms from an impurity. These atoms combine with the silicon atoms in such a way that electrons float around freely inside the silicon. This type of silicon is called *N-type* (or negative-type). The N-type silicon is the cathode of the diode.



### Semiconductor diode


See the "Schematic Diagrams" chapter to help you understand the illustrations in this section.

The other area of silicon also has an added impurity. But the atoms of this impurity combine with the silicon atoms in such a way that there is a shortage of one electron in the bonding. The absence of an electron is called a “hole,” and this hole can grab an electron from a neighboring atom. Thus, a hole can “float” from atom to atom the same way an electron might. The silicon with the holes is called *P-type* (positive).

For current to flow through the diode, the negative terminal of the battery must connect to the N-type silicon (the cathode) and the positive terminal to the P-type silicon (the anode). The negative terminal repels the free electrons of the N-type material. The electrons are forced toward the junction where they fill the waiting holes. However, as the electrons leave the anode, new holes form. This results in a constant flow of current from cathode to anode.

Current cannot flow in the opposite direction (see the illustration for the semiconductor diode). If the battery’s connection is turned around, it attracts the electrons and the holes away from the junction. Because there are no free electrons at the junction, no current can flow.

The **transistor** is perhaps the most important invention in the history of electronics so far. A transistor uses the P-type and N-type silicon in much the same way as a diode. However, the transistor has three electrodes, called the *emitter*, the *base*, and the *collector*. The collector is connected to the positive terminal of the battery, and the emitter is connected to the negative terminal. Electrons will try to flow from the emitter to the collector. However, a thin layer (the base) separates these two elements. If the base is negative, it repels the free electrons in the emitter. In this case, no current can flow from the emitter to the collector.

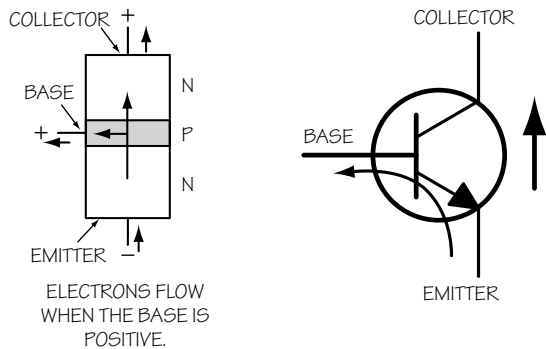


**NPN transistor**

If the base is positive, electrons can flow into the base from the emitter. Some of the electrons will flow into the positive base lead. But because the base is very thin, most of the electrons travel through the base to the collector. Thus, if the base is made more positive, more electrons will flow. Conversely, making the base less positive will reduce the current flow. You can see then that a small voltage on the base will control the amount of current through the transistor. For this reason, the transistor can be used as an amplifier in much the same way as a vacuum tube.

Notice the symbol in the illustration used to represent the NPN transistor. Another type of transistor is called the PNP transistor. Its structure and schematic symbol are shown in the following illustration. This transistor requires opposite polarity voltages for proper operation.

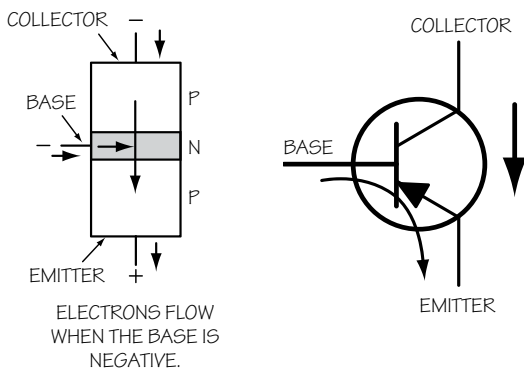NPN and PNP transistors are called *bipolar transistors*, and they are the most popular types used.



### PNP transistor

## Field Effect Transistor

The field effect transistor uses a single N-channel or P-channel with an insulated metal plate used to control current flow. Current enters the channel at the source lead and flows toward the drain lead at the other end of the channel. The voltage applied to the insulated plate, known as the gate, limits the current flow through the channel from source to drain. The most used FET is the metal-oxide semiconductor FET or MOSFET. An N-channel MOSFET will not conduct current if there is no voltage difference source to gate and

allow current flow when a higher voltage is applied to the gate (voltage difference with respect to the source pin). A P-channel MOSFET will conduct current if there is no voltage difference source to gate and allow current flow when a lower voltage is applied to the gate (voltage difference with respect to the source pin).

Complementary MOS or CMOS technologies use one P-channel MOSFET and one N-channel MOSFET connected such that the P-channel source pin connects to the circuit higher voltage (typically power supply) and connects the N-channel source to the lower voltage supply (typically 0-volt or ground). The drain of the two MOSFETs are connected and is the circuit output. The gates are tied together.

When the gates are connected to a low voltage (ground), the source to gate voltage of the N-channel is 0 volts so the channel transistor is “off” while the gate to source voltage of the P-channel FET is the “hi” voltage, so that transistor is “on” meaning the output voltage is connected to the power supply or high (for a low input). Conversely, if the two gates are tied to the higher voltage, the N-channel gate to source is now high, so it is “on” while the P-channel transistor gate to source is voltage is low, so it is “off.”

## Integrated Circuits

An *integrated circuit* (IC) is a complete circuit in a single package. Transistors, resistors, diodes, and capacitors can be formed in a single chip of silicon, a semiconductor. One chip can contain thousands or even millions of electronic components.

Integrated circuits have revolutionized many fields, including communications, information handling, and computing. They have reduced the size of devices, while providing faster speeds and increased reliability.

The individual components of ICs are extremely small and are assembled to a pattern that has been planned in advance. A chip might look flat, but it has several layers for circuits. Switches control the electrical current through the chip. The switches manipulate the binary code (discussed below) with “on” and “off” switches. The binary code is at the core of how a computer operates.



**The integrated circuit, or IC, has led to smaller electronic devices that are faster and more reliable.**

Chips come in many different sizes, with millions of transistors being able to fit on chips the size of a postage stamp.

Two basic types of IC are called *linear* and *digital*. Linear circuits include amplifiers, oscillators, regulators, and other circuits used in TV sets, audio amplifiers, radios, and hearing aids. Digital circuits include memories and arithmetic circuits and counters in watches, calculators, computers, and video games.

## Microprocessors

The microprocessor is a type of ultra-large IC. By 1971, the technique of making ICs had progressed to the point where enough computing power could be put on a single IC to form a tiny, primitive computer, or calculator. The first microprocessor was born. Today, microprocessors can incorporate more than a billion transistors, plus components such as resistors, capacitors, diodes, and wires.

The microprocessor accepts input data, modifies that data in some way, and produces an appropriate output. The earliest application of the microprocessor was the calculator. A calculator accepts numbers that the user enters on a keyboard, performs a mathematical operation on those numbers that the user desires, and then sends the result to a display. Today's microprocessors function as the central processing unit (CPU) of computers. They also are used in many electronics systems such as cameras, printers, planes, and automobiles.

The microprocessor in an automobile, for instance, examines inputs from several sensors, makes decisions based on those inputs, and adjusts such things as the mixture of air and fuel and the timing of ignition firing. The microprocessor's most important aspect is that it can be programmed to perform an almost limitless number of applications.

---

A computer might contain more than 2 billion transistors!

---

## Printed Circuit Boards

A printed circuit board (PCB) consists of a sheet of some type of insulator, a composite material classified as FR-4 made of woven fiberglass cloth with an epoxy resin binder. The FR-4 material is an insulator with copper traces printed or etched onto the FR-4 surface. The copper traces are implementations of the wire lines of the schematic drawing. Parts of traces may need to be routed from one side (layer) to the other side (layer). To connect the traces, feed-through holes are added to the circuit board.


Feed-through holes are drilled through the printed circuit board then filled with solder. The solder connects the copper of the top, bottom, and optional intermediate layers. Feed-through hole's solder is done during the fabrication of the circuit board.

Optionally, feed-through holes can be used to hold component leads. The feed through has a hole drilled through the solder for the component lead. The drilled hole is done during fabrication of the printed circuit board. The completed printed circuit board is now ready for insertion of the components drawn in the schematic.

A feed-through hole used for a component lead must be larger to allow room for the component lead diameter plus some insertion clearance of the lead into the hole. If no component lead is being inserted in the hole, the diameter of the feed-through hole can be much smaller and require less printed circuit board space.

Later, during the assembly process, a component lead is inserted into the hole and the hole and lead must be soldered together to make solid electrical contact.

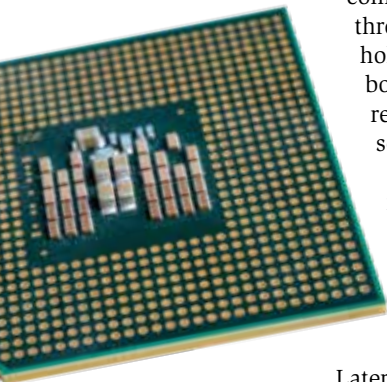Several layers of traces, separated by FR-4 sheets may be sandwiched together for more complex electronic designs with feed-through holes connecting the traces as needed.



**Surface-mount technology ball grid array (about 800 pins)**

## Through-Hole Technology

The technology used for placing component leads in holes drilled through the printed circuit board reached a practical limit when integrated circuits got over about 40 pins. A feed-through hole with space for the lead and the insertion tolerance meant that, based on PCB fabrication technologies at the time, integrated circuit leads needed to be about 0.100" apart. Various techniques were tried with larger IC packages including longer packages, the IC pins in a grid pattern and others. There was not a viable solution to reach what would eventually be today's package pin counts.

## Surface-Mount Technology

By removing the component pin from going through the feed-through hole, the feed-through could be much smaller and

Intel cofounder Gordon Moore wrote in 1965 that the number of transistors in integrated circuits doubled approximately every two years. This observation, called Moore's law, still holds true today.


moved away from the component. The component pins could be replaced with a square pad on the component and the printed circuit board would have a matching pad on the “out-side” copper layer. Without the constraint of the feed-through hole with drilled lead space, component pins could be placed much closer together or more pins could be placed around the former through hole package sizes. This change led to the very high pin count packages required for today's integrated circuits, such as the processor of your home computer.





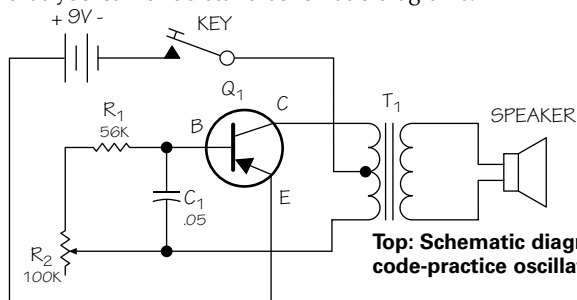
# Schematic Diagrams

The illustrations in the previous section didn't show you a picture of a real diode or transistor. Instead, they showed you a kind of illustrated outline, called a *schematic diagram*. These diagrams are a simple way of showing how electronic components are connected. In a schematic, symbols stand for the different electronic components. The schematic diagram illustrated here is for a code-practice oscillator, used to practice Morse code. The corresponding pictorial representation shows how the components actually look. In the schematic, a different type of symbol represents each type of component: long and short lines represent the battery; a zigzag line stands for a resistor. In this section, you will learn these symbols so that you can understand schematic diagrams.



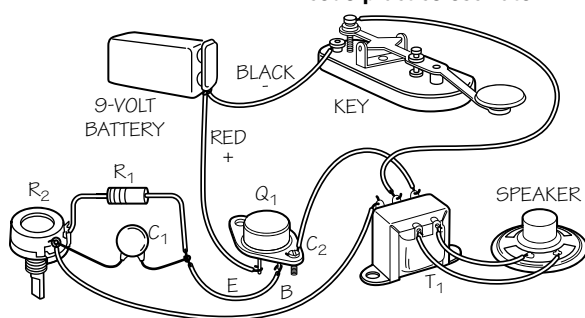
**Bottom: Pictorial representation, code-practice oscillator**



Notice that each component in the **schematic diagram** on this page has a reference designator such as 9V, Key, R1, R2, C1, Q1, T1. The designators also appear in the **pictorial diagram** to clearly show which component is which. These become more important in designs with many more components.

To start, compare the schematic diagram with the pictorial and match each symbol in the schematic with its equivalent component in the pictorial. Also match each line in the schematic with the appropriate wire in the pictorial. Notice where two lines cross in the schematic. If the wires are to be connected, a dot shows at the crossing on the schematic. If there is no dot, the two wires bypass each other and are not connected.

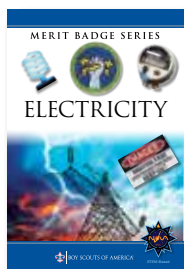When you draw your schematic for requirement 2, you will need a sharp pencil, paper, and a ruler or straight edge for drawing straight lines. A compass might be helpful for drawing circles. If you have a computer with a drawing program, you might use that to draw a schematic. There are also several freely available schematic capture tools.



---

To learn  
more, read  
the *Electricity*  
merit badge  
pamphlet.

---

## Component Types

Before we look at the most common types of electronics components, as well as the schematic symbol and a pictorial of each one, let's define and review some basic terms (also see the Basic Electronics Theory section):

- *Electricity* is a property that electrons have that causes them to behave in certain predictable ways.
- *Electrical charge* is a quantity of electricity.
- The *electron* is a tiny particle that has a negative electrical charge.
- *Current* is defined as the flow of electrons.
- *Voltage* is the pressure that causes current to flow.
- *Resistance* is the opposition to current flow.
- *Direct current* (DC) is current that always flows in the same direction.
- *Alternating current* (AC) is a current that reverses its direction of flow many times each second.
- *Frequency* is the number of times that a repeats its pattern in one second.

## Passive Components

**Fixed Resistor:** Each resistor has a specific amount of resistance. A resistor is like a nozzle on a water hose. For a given water pressure, the nozzle controls the amount of water that is allowed out of the hose. Similarly, for a given voltage, a resistor controls the flow of electrical current.

## Know Your Prefixes

This table lists some prefixes used in the electronics industry. An example term is given for each prefix; each prefix may be used with many other units of measure. For example, microsecond, microvolt microamp, microohm, microhenry, and microfarad all use the micro prefix to denote one millionth of the corresponding unit.


| Prefix | Abb. | $\times 10^n$     | Term          | Value               |
|--------|------|-------------------|---------------|---------------------|
| peta   | P    | $\times 10^{15}$  | 1 petabyte    | 1 quadrillion bytes |
| tera   | T    | $\times 10^{12}$  | 1 terabyte    | 1 trillion bytes    |
| giga   | G    | $\times 10^9$     | 1 gigawatt    | 1 billion watts     |
| mega   | M    | $\times 10^6$     | 1 megaohm     | 1 million ohms      |
| kilo   | K    | $\times 10^3$     | 1 kilovolt    | 1 thousand volts    |
| deci   | d    | $\times 10^{-1}$  | 1 decibel     | 1 tenth bel         |
| milli  | m    | $\times 10^{-3}$  | 1 milliamp    | 1 thousandth amp    |
| micro  | u    | $\times 10^{-6}$  | 1 microsecond | 1 millionth second  |
| nano   | n    | $\times 10^{-9}$  | 1 nanohenry   | 1 billionth henry   |
| pico   | p    | $\times 10^{-12}$ | 1 picofarad   | 1 trillionth farad  |

Most resistors are made of a carbon compound. Resistors used for high currents often are made from special wire that is wound on an insulating form. The type of compound or wire used determines how much electrical current can flow for a given voltage.

The value of a resistor is given in ohms. The symbol for the ohm is the Greek capital letter omega ( $\Omega$ ). Thus,  $1\Omega$  designates the resistance of 1 ohm. A  $1k\Omega$  resistor has a resistance of 1 kilohm, or 1,000 ohms. A  $1M\Omega$  resistor has a resistance of 1 megohm, or 1 million ohms.

The illustration below shows a variety of *fixed resistors* and a cross-section of a fixed resistor. The values of fixed resistors cannot be changed.


### Fixed resistor packages

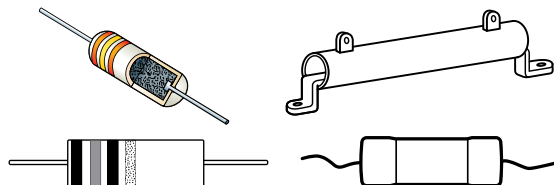


Schematic symbol

Older types of fixed resistors have bands of color that allow you to determine their resistance value. (See “The Color Code of Resistors” section on page 40.) The cross-section of this fixed resistor shows the inside, which is made of carbon. Note the schematic symbol for a fixed resistor.

**Variable Resistor:** The resistance of variable resistors can be adjusted. Rheostats are two-leaded devices that vary in resistance from 0 to the rated resistance value. Three-leaded variable resistors, known as potentiometers (pots), have a fixed resistance between leads 1 and 3, and have a resistance on lead 2 proportional to the amount of rotation on the adjustment arm. These variable resistors can be used in appliances that need their currents adjusted or when the resistance needs to be varied, such as with lights that can be dimmed.

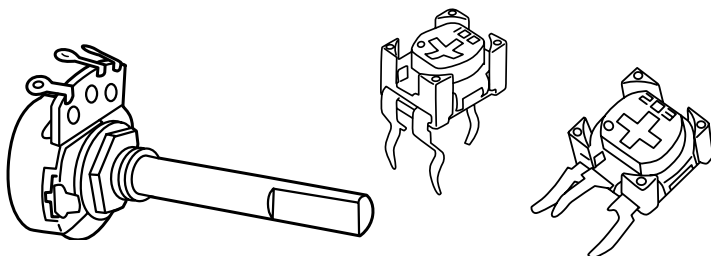


Variable resistor packages

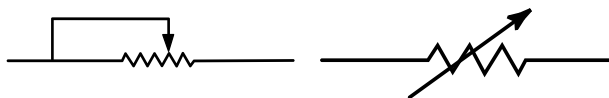


Schematic symbols

**Capacitor:** A capacitor is a storage element for electrical charge, similar to a bottle that stores a liquid. The basic unit of capacitance is the farad (F). Practical capacitors have capacitance values in microfarads ( $\mu\text{F}$ ). The physical size of a capacitor depends on its voltage rating and its capacitance value. The higher the voltage rating and the larger the capacitance value, the larger the capacitor must be.

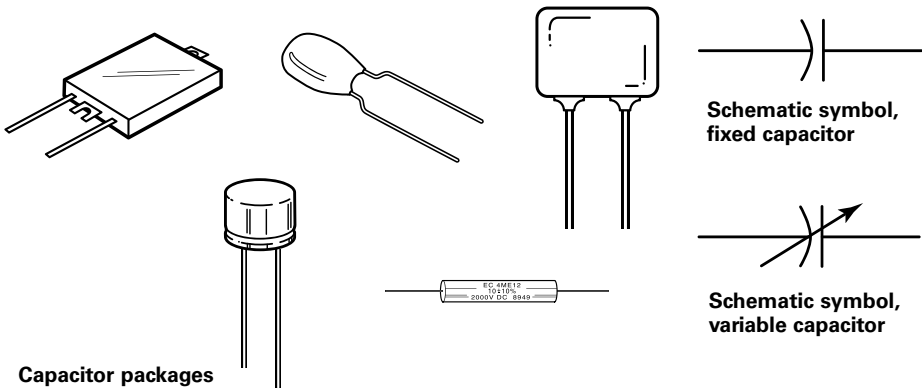
**Inductor:** An inductor is a coil of wire usually wrapped around some type of metal or hollow core material and is used to smooth out variations in the current flow. When current is applied to the coil, a magnetic field is established around the



core. When the current flow stops, the magnetic field begins to collapse and in doing so induces current back into the wire until the field has collapsed. The magnetic field tends to collapse at a rate that maintains the original current in the wire. Single coil configurations are generally called a **choke** whereas two or more coils can be configured either as a choke to filter current changes or as a **transformer** for changing voltage and current values.

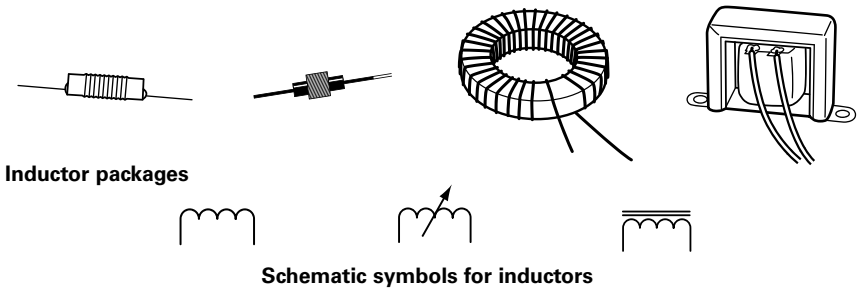


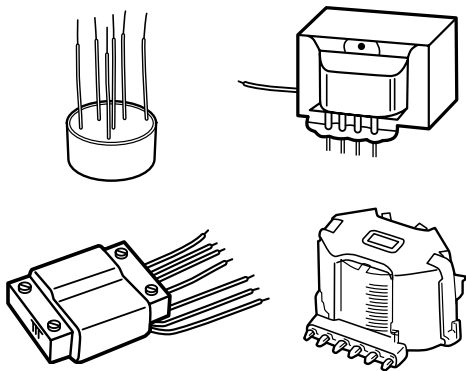**Transformer:** A transformer consists of two or more coils each with multiple turns of wire around the magnetic core. The primary coil is the coil where power is applied to the transformer and the other coils are referred to as secondary coil(s). The transformer uses the magnetic field established by current flow in the primary coil to induce a current in the



Transformer packages

Schematic symbols for transformers

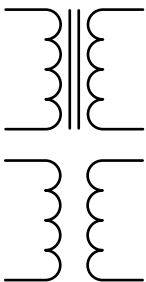


secondary coil(s). The ratio of turns from the primary to a secondary coil determines how much the incoming voltage is multiplied on the secondary side and how much the secondary current is divided by the primary current in the secondary. Because transformers operate on changing magnetic fields caused by changing current, transformers do not operate on direct current (DC) currents.

Semiconductor Devices

Semiconductor devices are typically made of silicon-based material. Diodes and transistors are two common semiconductor component types. Semiconductors come in various package sizes based on the amount of power they must dissipate in rated operation.

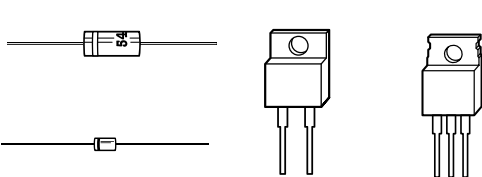**Diodes:** Diodes operate as check valves, passing current in one direction but not the other. A diode’s most common application is in power supplies. It changes alternating current (AC) into direct current (DC).




Diode packages


Schematic symbol: Standard diode



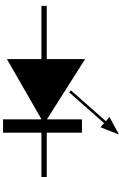Schematic symbol: Light-emitting diode (LED)



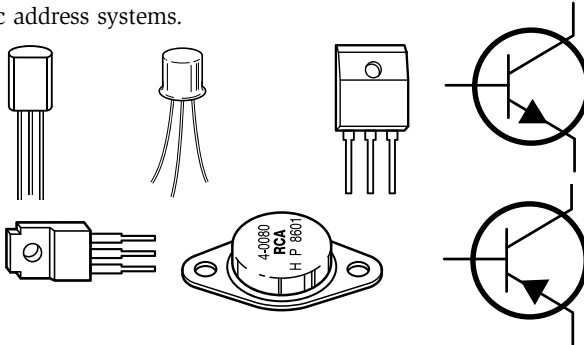**Transistors:** Transistors are solid-state devices used for controlling current. A very small input current controls a much larger output current. For example, the small current from a microphone can control a much larger current that drives a loudspeaker. This is the idea behind the audio amplifiers used in public address systems.




Transistor packages

Schematic symbols
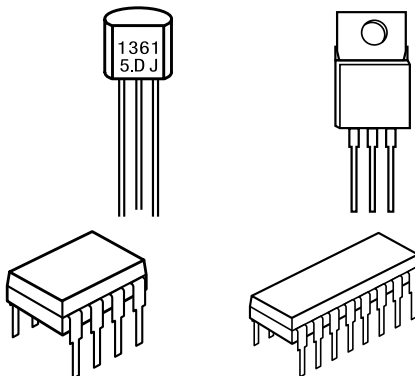
## Integrated Circuits (ICs)


Complex circuits are available in integrated circuit (IC) form at inexpensive prices. The IC, which typically consumes little power, is reliable, cheap, and small. Because devices using ICs can be improved and made cheaper, the IC has replaced traditional components in many applications. As shown here, ICs come in several types of packages. The dual in-line package (DIP) is the most popular style for most hobby applications. Schematic symbols for ICs are typically very function-specific.



Integrated circuit packages
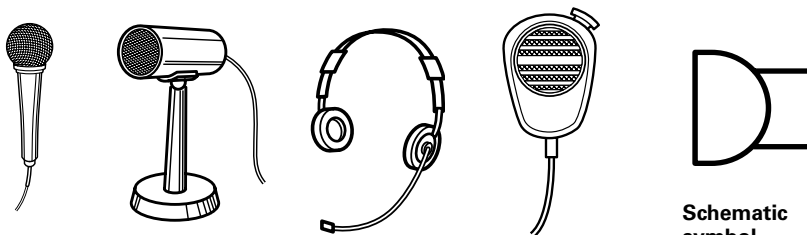
## Electromechanical Components


**Microphone:** A microphone changes sounds into electrical impulses. Either a thin, flexible disk (a diaphragm) or a crystal in the mike vibrates whenever sound strikes it. The vibrations are changed into small electrical signals. These signals typically need to be amplified before they are usable.



**Schematic  
symbol**


**Speaker:** A speaker then converts the electrical impulses back into sounds. An electromagnet moves a speaker cone based on the incoming audio signal. The speaker cone moves the air around and it which causes the audio sound to spread across the space and recreating the original sound.

### Speakers

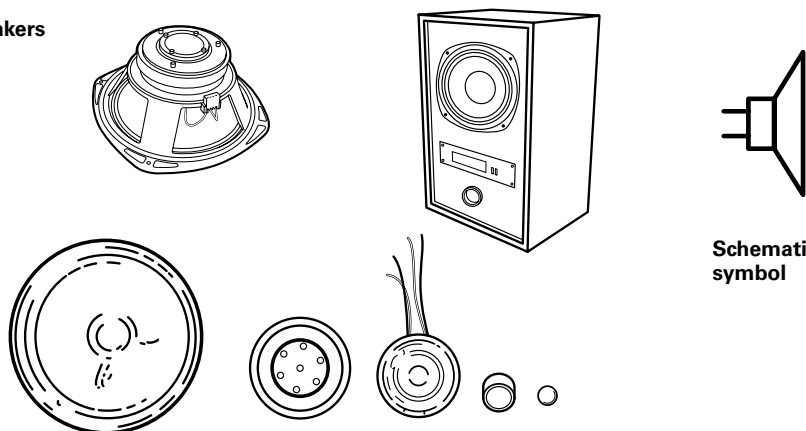

**Schematic  
symbol**

**Switches:** are an important part of almost all electronic equipment. They come in a wide variety of shapes, sizes, and functions. Switches are categorized by the number of circuits they switch (single, double, triple, etc.) and then by the number of switch position contacts. A switch may have an output contact for each position of the switch. The switch will typically have a default position. A circuit that makes contact in that position is called a Normally Closed (NC) contact or in drawing below from terminal A to C. If the switch is moved out of default position, and makes contact with an electrical terminal, that position is called Normally Open (NO) and is shown as connections A to B in drawings below).

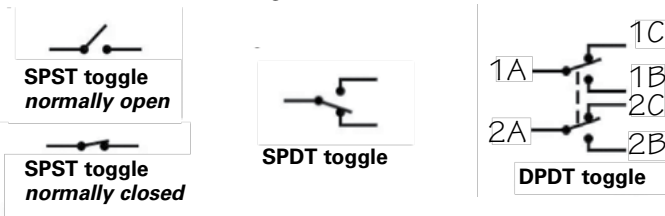


The simplest is the *single-pole, single-throw* type. When closed, this switch completes a circuit, allowing an electric current to flow. When it is open, the circuit is broken, and the current does not flow. The on-off switches on most electronic devices are of this type (above left).


A *single-pole, double-throw* switch has a contact arm that can be set in either of two positions. In the example shown here, terminal A can be connected to either terminal B or terminal C. The dashed line between the switches shows the mechanical connection (above center).

A *double-pole, double-throw* switch can simultaneously switch two wires from one circuit to another. It can be thought of as two single-pole, double-throw switches that operate together (above right).


A *rotary* or *selector* switch has one or more arms (poles) that can be set to various positions. A single pole 10-position switch is shown below. Notice that the terminal at the very bottom connects the signal to the rotatable arm.

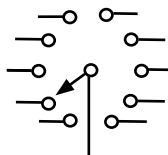**Switches come in many sizes and shapes, so only schematic symbols are shown here.**



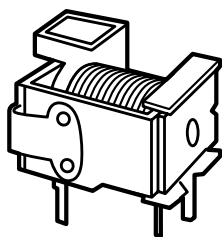

Relay package

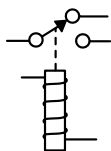

Schematic symbol

**Relays:** A relay is a magnetically operated switch. It has a wire coil wrapped around an iron core forming an electro-magnet. When current flows through the coil, a magnetic field develops. The magnetic field attracts a movable part called an armature, which moves all relay switch poles from normally Closed (magnet off) to Normally Open (magnet energized).


A relatively small current can cause the switch contacts to close, but the contacts can handle a much heavier current. The relay allows a small current to switch higher current(s) on or off. By using several contact sets (single, double, triple or more poles and single or double throw). A multi-pole relay allows a single control (coil) current to control several different currents simultaneously.

## Chemical Components


**Batteries:** Batteries are made from several types of materials for different uses. Alkaline, lithium, and mercury batteries are used when long life is desired. Nickel-cadmium batteries give shorter service but can be recharged. The nickel-metal hydride battery is replacing the nickel-cadmium battery because it doesn't suffer the memory effect (that is, not allowing a partially charged battery to fully recharge before use). Lithium-Ion type batteries have replaced many of the older battery types. Zinc-carbon also is used in many inexpensive dry-cell batteries.




Most electronic circuits and products operate at low supply voltages and have low power requirements. These devices are often driven from small batteries or DC voltage sources. Depending on the type of product, a coin battery, one, two or four flashlight batteries are often adequate for relatively long service.

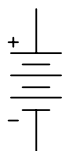Ordinary flashlight dry cells produce approximately 1.5 volts. Four 1.5-volt cells connected in a series can provide 6 volts. Single 9-volt batteries also are used.



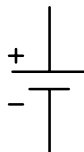**Batteries come in many sizes and shapes, so only schematic symbols are shown here.**



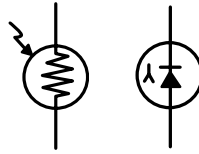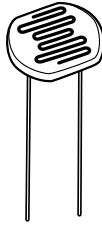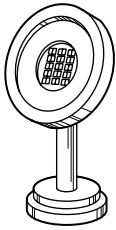

Schematic symbols

### Photoelectric cells


**Photocells:** A photoelectrical cell changes one or more of its characteristics when exposed to light. It is popularly called the electric eye, which controls operations such as traffic lights, door openers, and devices that activate lights at dusk and turn them off at dawn. One type of photoelectric cell is called a photoconductive cell. Another name for this type of cell is the light-dependent resistor (LDR). This special resistor has a small window so that light can strike the resistance material. Generally, such a cell has a high resistance when in darkness. Another type is called a photovoltaic cell. This is the familiar “solar cell” that is used to power electronic equipment on spacecraft. It produces a low voltage across its terminals when exposed to light, especially sunlight, thus converting light energy into electrical energy.

**Other Component Types:** There are many other types of components used in electronics but these are the more common components that a hobbyist is likely to use.

The development of electronics has benefited our daily lives in many ways, including the protection of life and property. Today, electronics and electronic circuits play a vital role in the security field.

Whether it's a burglar alarm motion sensor, door contact, or the alarm panel and communication devices, closed circuit television (CCTV), or devices related to detecting smoke and fire, electronics is what makes it all happen.

## The Color Code of Resistors

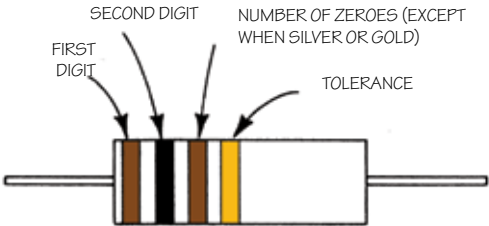

**Resistors are labeled with colored bands. The colors of the bands represent numbers that determine a resistor's value. The fourth band represents the resistor's tolerance.**

The *value* of a resistor is specified in ohms and is indicated by colored bands around one end of the resistor. The electronics industry devised this system because small printed numbers would be too hard to read or might be concealed by the position of the resistor.

Most resistors have four bands, with the first three (counting from the end of the resistor) indicating the value in ohms. The fourth, which is either silver or gold, indicates the tolerance (discussed below). Colors used for the bands are used in place of numbers. To determine the resistance value in ohms, examine the color bands starting with the one closest to the end of the resistor.

If you need help remembering the order of the colors in this chart, you can memorize this simple sentence, in which each word begins with the same letter as the color: *"Better Be Right Or Your Great Big Venture Goes West."*


| Color  | First Band | Second Band | Third Band* |
|--------|------------|-------------|-------------|
| Black  | —          | 0           | —           |
| Brown  | 1          | 1           | 0           |
| Red    | 2          | 2           | 00          |
| Orange | 3          | 3           | 000         |
| Yellow | 4          | 4           | 0,000       |
| Green  | 5          | 5           | 00,000      |
| Blue   | 6          | 6           | 000,000     |
| Violet | 7          | 7           | 0,000,000   |
| Gray   | 8          | 8           | 00,000,000  |
| White  | 9          | 9           | 000,000,000 |

\*Add this many zeroes after the first two numbers.

Suppose a resistor has a brown, a black, and then a brown band. The code chart shown here tells you that brown represents the number 1. The second black band represents the number 0. The third band tells you how many zeroes to add to the first two numbers. In the example, the band is brown, so you add one zero. Therefore, the value of this resistor is 1-0-0, or 100 ohms.

Now try the example for the resistor shown here, which has a red band first, then a yellow band, and then an orange band. The red band means that the first number is 2. The yellow band corresponds to the number 4. The orange band tells us to add three zeroes. Thus, the value is 2-4-000, which translates to 24,000 ohms, or 24 kilohms (k $\Omega$ ).

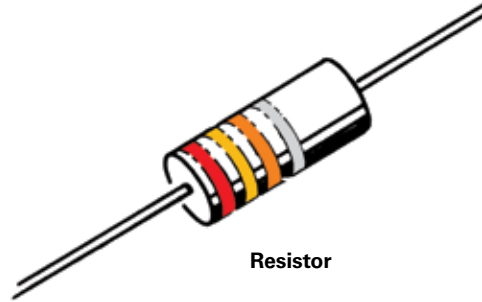Most surface mount components are too small for color bands, so the color bands are converted back to digits and printed onto the top of the resistor as 243 for 24,000 ohms, or 24 kilohms (k $\Omega$ ).



**Resistors in an old radio**



# Soldering

Before you begin working with a circuit, read and study this chapter on soldering. Anyone working in electronics must know how to solder well, and safely. It takes practice, but once you learn, you will be able to properly assemble an electronics project.

**Review the “Soldering Safety” tips on the next page before you begin your soldering work on requirement 3.**

In all electronics work, the wiring connections must be absolutely secure. A loose connection in a radio, for example, could result in noise, scratching sounds, or no sounds at all. Poor connections in a TV could disrupt the sound and picture. And beyond just a radio and a TV in someone’s home, the safe operation of airplanes and the lives of astronauts in flight depend on secure electronics connections.

Soldering is not just gluing metals together like you glue together pieces of wood. Done correctly, soldering *unites* the metals so that electrically they act as one piece of metal. You do this with a mixture of lead and tin solder and a soldering iron.



---

Soldering surface mount components is not covered in this pamphlet. With parent or guardian's permission, search online for "how to solder surface mount components" to learn how.

---



## Soldering Safety Tips

- Solder only under the constant supervision of a responsible and knowledgeable adult.
- Make sure that the power is off on the project being soldered.
- Certain kinds of solder release fumes that can be harmful to your eyes and lungs; therefore, always work with solder in a well-ventilated area.
- Do not allow anyone to drink, eat, or smoke in the soldering area.
- Wear safety goggles when soldering.
- Before you start soldering, protect any flammable material with a fireproof shield or wet rags, and have a fire extinguisher nearby.
- Be careful not to let hot solder splash around because it will burn you almost instantly.
- If possible, use a soldering iron stand or clamps when you are soldering, leaving one hand free to hold the solder.
- Don't overheat components, circuit boards, or plastic wires when soldering.
- *Oxidation* (rust) develops more rapidly when a soldering iron is hot, so try to make sure the iron doesn't stay hot for long periods of time.
- Never touch the tip of a hot soldering iron; keep the iron in a holder when you aren't using it. Don't lay it down on your bench or work area.
- Never leave a soldering iron on unattended.
- When you are finished soldering and cleaning up, thoroughly wash your hands.

## The Soldering Iron

An inexpensive pencil-type soldering iron of no more than 40-watt capacity (15 to 25 watts are also suitable) is the best for electronics work. The tip should be 1 to 2 millimeters (mm); the solder should be 1 mm. It is helpful to get an iron with interchangeable tips of different diameters or shapes to be used on different kinds of work. The iron should be well-balanced and have a handle that will remain cool while you work.

**Tinning your iron** means coating the tip of the solder iron with a thin coat of solder. If your iron is new, read the instructions about preparing it for use. Most new irons are already tinned, so you might not have to tin it. If the tips are silvery, you can use them as they are.

If instructions aren't included with your iron and the tip is not silvery, first use a fine file to file the tip until it is shiny. Then heat the iron and coat the tip with rosin-core solder. Be sure to coat all sides of the tip.

If you have an older iron that has been used and the point is already silvery, just wipe it clean with a cloth and you are ready for work. If it is dull or looks coppery, file and tin it.

You also should have a heat-resistant bench-type iron holder so that the hot iron can safely be set down between uses. Look for one that has a holder for tip-cleaning sponges.

## How to Solder

A well-soldered joint, one that will be reliable in use, will be nice and shiny looking. To achieve a well-soldered joint, make sure you do the following:

1. Solder with a clean, well-tinned tip. Wipe the tip on a damp sponge before soldering and between soldering.
2. Make sure all wires, parts, and the circuit board to be soldered are clean.
3. Make a good mechanical joint before soldering.
4. Allow the joint to get hot enough before applying solder, then apply an adequate amount of solder to the joint. Only heat the joint with the solder iron, not the solder itself. When you touch the solder to the joint, the solder will flow onto the joint.
5. Allow the solder to set before handling or moving soldered parts.

If you take the time and make the effort to solder a perfect joint, you might save a lot of time later in trying to troubleshoot problems with your circuit.

Remember that in **preparing work for soldering**, dirt is the enemy of soldering. A solder will not take if parts are dirty, so be sure to completely clean all wires and surfaces before applying solder. Use fine sandpaper or emery paper to clean flat surfaces or wire. If you do have dirty parts or a dirty surface, you might try to use too much heat to force a connection.

Remember that no amount of cleaning will allow you to solder to aluminum. When making a connection to a sheet of aluminum, you must connect the wire by a solder lug or a screw.

When preparing wires, remove the insulation with wire strippers or a hobby knife. If using a knife, hold the knife at an angle as if you were sharpening a pencil. Do not cut straight into the insulation because you could nick the wire and weaken it. For enameled wire, use the back of the knife blade to scrape the wire until it is clean and bright.

Next, tin the clean end of the wire. Hold the heated tip of the soldering iron against the undersurface of the wire, and place the end of the rosin-core solder against the upper surface. As the solder melts, it will flow on to the clean end of the wire. Hold the hot tip of the iron against the under surface of the tinned wire and remove the excess solder by letting it flow down the tip. When properly tinned, the exposed surface of the wire should be covered with a thin, even coating of solder.

Before you begin, secure your work so that it won't move during soldering. With circuit boards, you could use holding frames. Use a modeler's small vice to hold other parts.

Unless you are creating a temporary joint, the next step is to **make a good mechanical connection** between the parts to be soldered. For instance, wrap the wire carefully and tightly around a soldering terminal or soldering lug. (Bend wire and make connections using long-nosed pliers.) When connecting two wires, make a tight splice before soldering. Once you have made a good mechanical contact, you are ready to solder.

When you are working with an ordinary circuit board, you will bend the wires of a component through the board. For those parts, such as some resistors, that become hot when in operation, raise them slightly above the board to allow some air circulation.

The next step is to apply the soldering iron and **solder to the connection**. The temperature of all the parts that are being soldered should be raised to about the same degree before applying the solder. If soldering a spliced wire, hold the iron below the splice and apply solder to the top of the splice. If the tip of the iron has a bit of melted solder on the side held against the splice, heat is transferred more readily to the splice, and the soldering can be done more easily. Don't try to solder by applying solder to the joint and then pressing down on it with the iron.

It usually takes two to three seconds to solder on a printed circuit board. Remember: Too much solder on a joint might cause short circuits with adjacent joints. However, if you don't apply enough solder, you might not form a secure and fully working joint.

When soldering the wires of a component, you might snip the extra wire leads off before soldering. However, with some components, such as semi-conductors, it might be best to snip the surplus wire after you have made the joint.

Don't disturb the soldered joint until the solder has set. This might take several seconds, depending on the amount of solder used to make the joint. Then take a good look at the joint. It should have a shiny, smooth appearance. It should not be pitted or grainy. If it is, then reheat the joint, scrape off the solder, clean the connection, and start over.



**Attach the wire to a soldering terminal or soldering lug.**



**Heat the wire and the lug.**



**Apply solder to both the tip and the connection.**



**Let the connection harden before moving the wire. Check for a smooth, bright joint.**



**Poor connections look crystalline and grainy, or the solder tends to blob.**




After the solder is well set, pull slightly on the wire to see whether it is a good, tight connection.
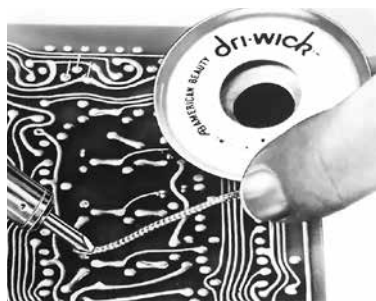
## How to Desolder

In case you accidentally make a wrong connection or have to move a component that has been placed incorrectly, you should learn how to desolder connections. Take care when desoldering to avoid breaking or destroying good parts. The leads on components such as resistors or transistors and the lugs on other parts might sometimes break off when desoldering a good, tight joint. To avoid heat damage, use as much care in desoldering delicate parts as you do in soldering them.

There are two ways to desolder. The first and usually easiest way is to use a metal wick or braid on a small dispenser reel to remove the melted solder. This braid is available at most electronics parts stores. Place the braid against the joint that you want to desolder. Use your heated soldering iron to gently press the braid against the joint. As the solder melts, it is pulled into the braid. Don't let the joint cool while the braid is resting against the joint. By repeating this process, you can remove virtually all the solder from the joint. Then reheat the joint and lift off the component leads.



**Desoldering braid**

The second method involves using a desoldering pump, or a vacuum device, to suck up the molten solder. Most electronics parts stores have these devices. Follow the manufacturer's instructions for the pump you are using, but here are some general guidelines. Use your soldering iron to heat the joint you want to desolder until the solder melts.

Then push down on the top of the pump to remove the air inside. Next, quickly place the tip of the pump on the melted solder you want to remove and press the button on the side. This will cause the pump's plunger to rise rapidly and create a vacuum inside. The rush of air at the tip of the pump will pull the melted solder in. Repeat until you have removed most of the molten solder. Then reheat the joint and gently pry off the wires.

Experiment with and practice your soldering techniques to fulfill requirement 3 before you begin working on your circuit. Use pieces of wire or some old components and wire. Practice until you can solder joints that are smooth, shiny, and tight. Then practice desoldering some of the connections until you are satisfied that you can do them quickly and without breaking wires or lugs.

**Remember these things  
when desoldering:**

- Be sure there is a little melted solder on the tip of your iron so that the joint will heat quickly.
- Work quickly and carefully to avoid damaging parts with heat. Use long-nosed pliers to hold the leads of components just as you did while soldering.
- When loosening a wire head, be careful not to bend the lug or tie point to which it is attached.




**Desoldering  
pump**

It's important to responsibly dispose of solder waste, which should be either recycled or treated as hazardous waste because it contains lead. It cannot be disposed of in your regular trash collection bin. As you desolder, collect the waste in a container clearly marked as solder waste—including the solder from your sponge or work towel. Throw your sponge or towel away. Contact local authorities for information about the proper disposal of solder waste in your area.




If you happen to get burned while soldering,

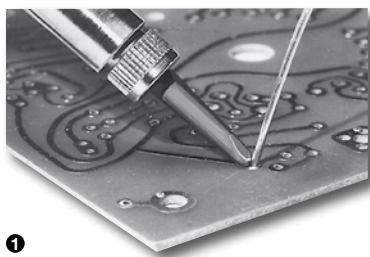
- Quickly cool the burned area with cold running water, an ice pack, or something frozen (such as a bag of peas) until the pain is gone.
- Apply a sterile dressing to help protect against infection.
- Do not apply any ointments or lotions.
- Seek medical advice from your doctor if the burn is severe.



1

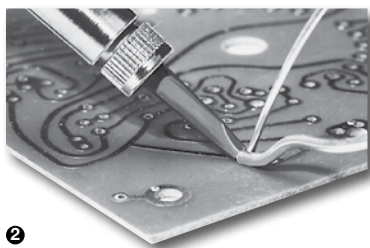

2

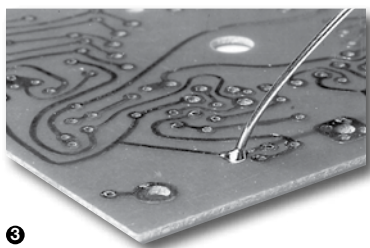

3

## Soldering Printed Circuit Boards

Most electronic devices use one or more printed circuit (PC) boards. A PC board is made of a nonconducting material, such as a thin sheet of fiberglass or phenolic resin (plastic) that has a pattern of foil conductors “printed” on it and has predrilled holes designed to hold components. You insert component leads into the holes and solder the leads to the foil pattern. This method of assembly is widely used, and you probably will use it if you choose to work with an electronics kit.

Printed circuit boards make assembly easier. First, insert component leads through the correct holes in the board. Mount the parts tightly against the circuit board unless otherwise directed. Insert a lead and then bend it slightly outward to hold the part in place. Then follow these steps.


**Step 1**—Touch the tip of your soldering iron to both the component lead and the foil until they are uniformly hot enough to melt the solder.

**Step 2**—Apply a small amount of solder to both the tip and the connection.


**Step 3**—Remove the iron and let the solder set before moving the wire or the board. The finished connection, as you have learned, should be smooth and shiny.

**Step 4**—Finally, clip off the excess wire length.

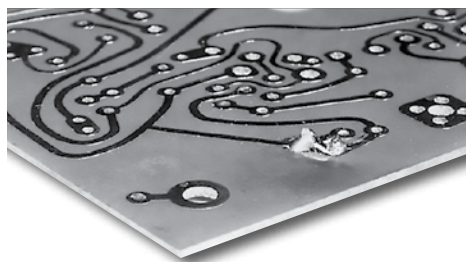Occasionally a solder “bridge” will form when solder connects between two adjacent foil conductors. You must remove such bridges or a short circuit will exist between the two conductors and the circuit won’t function properly. Remove the bridge by heating it with your soldering iron and quickly wiping away the melted solder with a soft cloth.



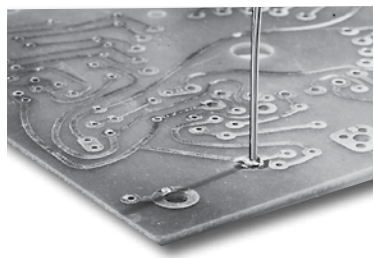Be sure to remove all solder “bridges,” which can cause short circuits.



A hole on the board could get plugged by solder. Clear the hole by heating the solder while pushing a component lead through the hole from the other side of the board.

## Caring for Your Soldering Iron

- Keep your soldering iron cleaned and well-tinned.
- Keep a damp cloth or sponge on your workbench. Before soldering a connection, wipe the tip of the iron across the damp cloth or sponge and then touch some fresh solder to the tip.
- The tip eventually will become worn or pitted. Repair minor wear by filing the tip back into shape. Be sure to tin the tip immediately after filing it. If the tip is badly worn or pitted, replace it.
- Oxidation forms on the tip rapidly when the iron is hot, so don’t keep the iron heated for long periods when you aren’t using it.
- Don’t try cooling the iron rapidly with ice or water. This could damage the heating element, and water might get into the barrel and cause rust.



# Control Devices

An important application of electronics is the control of certain operations with the use of *control devices*. For example, control devices can make lights go on at certain times or open doors automatically. To satisfy requirement 4, you will build a working electronic circuit. You may choose to build a control device.


Allow several days to find and buy the necessary parts before you start building your circuit. See the resources section in the back of this pamphlet for information about suppliers.

## Building a Control Device From Scratch

You can build a control project from a kit, but you may want to build a project from scratch. The one shown is easy to build and fun to use. It is a control circuit that uses light to control an audible alarm. This is a popular type of control circuit. It could be used to detect when the sun is shining so you can turn out your lights and save power.

The circuit is constructed on the single piece of 3-by-4-inch perforated board. While the exact size is not critical, a board that is too big is better than one that is too small. The holes in the board need to be  $\frac{1}{10}$  inch apart. This is necessary so that the pins of the op amp will fit.

Many types of boards are available. The board used (and shown in the photographs) for this project has foil patterns designed especially for integrated circuits, which makes the project easier. To use this type of board, insert components through the board from the top and solder to the foil patterns on the bottom of the board. You make connections from one component to the next by using short wires called *jumper*s.

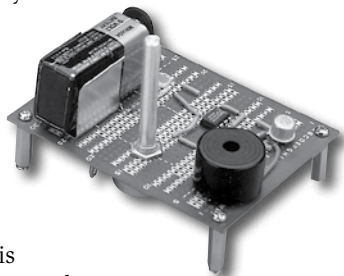

**This control circuit uses light to control an alarm.**

## Parts Needed

- ☐  $R_1$  100 k $\Omega$  potentiometer
- ☐  $R_2$  100 k $\Omega$  resistor
- ☐  $R_3$  10 k $\Omega$  resistor
- ☐  $R_4$  4.7 k $\Omega$  resistor

**Note:**  $R_2$ ,  $R_3$ , and  $R_4$  can be 5 percent or 10 percent tolerance and either 1/2 or 1/4 watt.

- ☐ LDR Light-dependent resistor, cadmium-sulfide photocell
- ☐  $Q_1$  NPN transistor type 2N3053
- ☐ IC<sub>1</sub> 741 operational amplifier (op amp)
- ☐ PB Piezoelectric buzzer
- ☐  $S_1$  Single-pole, single-throw switch
- ☐ Perforated board approximately 3  $\times$  4 inches (described on page 53)
- ☐ Four standoffs (legs) and screws
- ☐ Battery holder for 9-volt battery
- ☐ 9-volt battery
- ☐ Battery clip for 9-volt battery
- ☐ 4 feet of No. 24 insulated wire

## Procedure

To build this circuit, follow these steps.

**Step 1**—Gather the parts. You may be able to buy parts at an electronics supply store, but more easily today you can purchase electronic components online (see the resources section at the back of this book). It's a good idea to make sure you can find all the parts before you buy any of them. This circuit will work with a wide variety of parts.

**Step 2**—Lay out the circuit board. Before you begin, decide where each component will go on the board. The illustration here shows a suggested layout. Lay the components on the board and trace the outline of each to make sure everything will fit properly.

**Step 3**—Drill the holes. You must drill several holes (see the illustration for the pattern) in the circuit board before mounting any components. The four holes at the outer corners are for the four standoffs, or legs, that will hold the circuit board. It is recommended that you buy a board that has these four holes already drilled. This will leave you with only three holes to drill. The first is the small hole for the battery holder. Make this hole slightly larger than the screw that holds the battery holder to the board. Two larger holes are required for the potentiometer and the switch. In each case, make the hole slightly larger than the part that is to be inserted through it. Drill the holes carefully so you don't damage the perforated board.

**Step 4**—Mount the IC. Attach the 741 op amp first. It must be mounted so that its pins are attached to foil patterns that allow additional components to be attached. Insert the IC in the top of the board.

Identify pin 1 of the 741 Op amp IC as illustrated on the top of the next page. Mark pin 1 on the board with a pencil so that it is easier to identify each of the pins as you solder components to them.


**Step 5**—Mount the LDR. Insert the leads of the light-dependent resistor into the board at the location shown and solder the leads to the foil. Don't worry about which lead is which. The LDR can be turned either way.

**Step 6**—Mount  $R_2$ ,  $R_3$ , and  $R_4$ . Insert the leads of the resistors at the locations shown. Bend the leads over so that you can insert them through the board and solder them to the bottom side. Don't worry about which lead is which. The resistors can be turned either way.


**Step 7**—Mount the transistor. Insert the transistor ( $Q_1$ ) into the board, carefully observing the emitter, base, and collector connections. The drawing illustrating the 2N3053 transistor seen at the bottom of the page shows how to identify the three elements.

**Step 8**—Mount the buzzer. Insert the buzzer (PB) through the board. Note that the minus (-) and plus (+) sides must be connected as shown in the schematic.


**Step 9**—Mount the switch. First remove the retaining nut. Mount the switch by pushing it through from the bottom of the board. Attach it to the board with the retaining nut. Cut two lengths of wire, each about 3 inches long. Remove  $\frac{1}{4}$  inch of the insulation from each end of the wire. Turn the board upside down and connect the center switch post to a foil pattern using a prepared wire and one of the side of the switch posts to another foil pattern using the other wire.

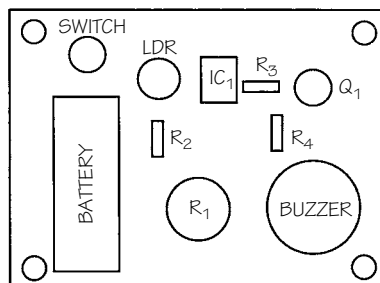


**Suggested layout**

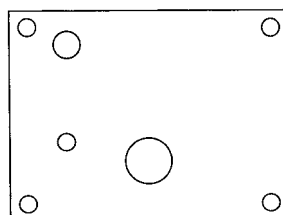


**Hole pattern**

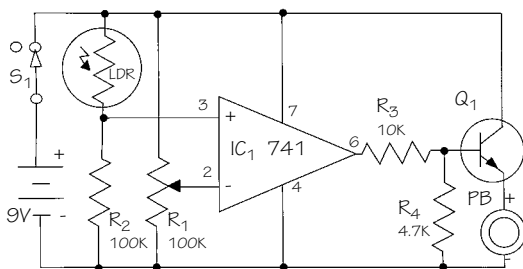

**Schematic diagram, circuit board**

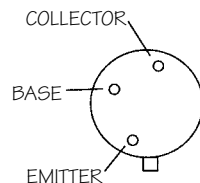

**2N3053 viewed from bottom**

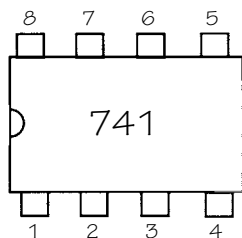

Viewed from top

**Step 10**—Mount the potentiometer. Remove the retaining nut. Mount the potentiometer ( $R_1$ ) by pushing it through from the bottom of the board. Attach it to the board with the retaining nut. Cut three lengths of wire, each about 3 inches long. Remove  $\frac{1}{4}$  inch of insulation from each end of the wire. Turn the board upside down and connect the potentiometer lugs to the foil patterns by using the three prepared wires as seen in the top view shown here.

**Step 11**—Mount the battery holder.

**Step 12**—Mount the battery clip. Strip  $\frac{1}{4}$  inch of insulation from the ends of the battery clip's black and red leads. Solder the black and red leads to the board. Do not connect the battery yet.

**Step 13**—Interconnect each of the components using small jumper wires, being sure each wire is electrically connected between the correct components. A good way to do this is to refer to the schematic and color each line on the schematic as you connect that jumper wire on the board. Cut each wire to the length needed and remove  $\frac{1}{4}$  inch of insulation from each end of the wire. Insert the jumper from the top of the board and solder to the foil on the bottom.

**Step 14**—Check all wiring. Before you apply power, recheck all wiring as described in the soldering section. Make certain that all components are interconnected properly. Check the pins of the op amp to make certain that you have the pin numbers right. Also recheck the placement of the transistor ( $Q_1$ ).

**Step 15**—Apply power. Attach the battery clip to the battery. If the buzzer sounds, flip the on-off switch to the opposite position. Place the battery in the holder.

**Step 16**—Coarse-adjust  $R_1$ . Flip the on-off switch to the "on" position. If the buzzer does not sound, adjust the potentiometer until you hear a sound from the buzzer. If you cannot make the buzzer sound by turning the potentiometer, flip the switch in the "off" position and adjust the potentiometer until the buzzer sounds. If the buzzer will not sound in either switch position, then immediately disconnect the battery and recheck all wiring. Correct the problem by rewiring as necessary. Repeat the process until you hear a tone from the buzzer.

**Step 17**—Fine-adjust  $R_1$ . Once you get a sound from the buzzer, cover the LDR with a finger to block light from the device. With the LDR covered, back off the setting of the potentiometer just to the point where the buzzer no longer sounds. The buzzer should now sound when the LDR is uncovered but *stop* buzzing when the LDR is covered. The circuit is detecting the presence of light and responding by sounding the buzzer.

### Circuit Operation

To understand how the circuit works, refer to the schematic diagram shown on the previous page. Start at the buzzer (PB) and work backward. The buzzer will sound when current flows through it. Transistor  $Q_1$  controls the current through the buzzer. When  $Q_1$  conducts, current flows through  $Q_1$  and the buzzer, creating the sound. In turn, the 741 op amp controls  $Q_1$ . The 741 ( $IC_1$ ) is an integrated circuit that contains dozens of transistors connected as a very high-gain amplifier. This means that it can amplify extremely tiny differences in the voltages applied to the two input terminals (pins 2 and 3).

The resistance of the light-dependent resistor (LDR) determines the voltage on pin 3 of the op amp. If no light strikes the LDR, the resistance across the LDR is high, which causes the voltage at pin 3 of the op amp to be low. When light hits the LDR, its resistance falls and the voltage on pin 3 of the op amp increases.


Before using the circuit, in steps 16 and 17, you adjusted the setting of  $R_1$ . Moving the arm of  $R_1$  changes the voltage at pin 2 of the op amp. With the LDR shielded from light, you set  $R_1$  just below the point at which the buzzer is activated. When  $R_1$  is properly set, the voltage at pin 3 is slightly lower than the voltage at pin 2. The op amp amplifies this tiny difference in voltage and produces a very low voltage at its output. This low output voltage holds  $Q_1$  cut off so that no current can flow through the buzzer.

When light hits the LDR, as was noted, its resistance drops. This increases the voltage at pin 3 of the op amp. The op amp amplifies this difference, producing a high voltage at its output. This turns  $Q_1$  on, forcing current through the buzzer and sounding the alarm.


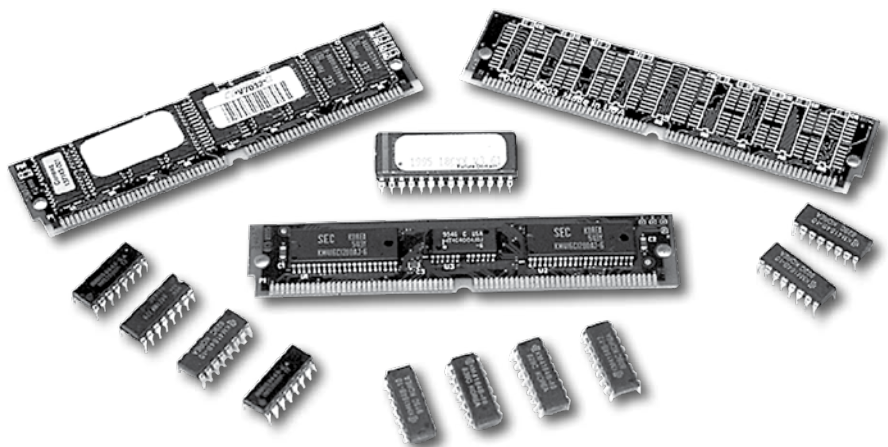
# Digital Electronics

Since the use of transistors began in 1948, the field of electronics has undergone a revolution that continues to allow for the introduction of a vast array of new devices. The development of digital electronic components has revolutionized fields such as computing, communications, and information handling. Such components have replaced many traditional circuits and components.



Possibly the best example of this revolution is the personal computer and related products. Other examples are digital watches, digital thermometers, hand-held computers and games, complex calculators, electronic games, televisions, and digitally recorded music and videos.

## Binary Number System

To understand digital electronics, you must first learn the *binary* number system, which is used in digital equipment. The *decimal* system of numbering uses 10 different digits: 0, 1, 2, 3, 4, 5, 6, 7, 8, and 9. This number system is suitable for people but is too complex to be used by electronic circuits. Digital logic is a simple process that can make only two decisions: true or false. So the binary number system has only two digits: 0 and 1. Thus, “true” can be represented by 1 and “false” by 0.

With only two digits, how are numbers larger than 1 represented? The answer is the same way numbers greater than 9 are represented in the decimal system. In the decimal system, the highest single-digit number is 9. We represent numbers greater than this by using two or more digits in combination. That is, 10 is represented by using the digits 1 and 0 together.

In the binary system, the highest single-digit number is 1. To represent numbers greater than this, we again use two or more digits in combination. The number 2 cannot be represented by the symbol “2” because this digit is not used in the binary system. Instead, the digits 1 and 0 must be used together, to form 10. Therefore, in the binary system, 10 represents the number 2 and not the number “ten.” The number 3 is represented by the next larger two-digit number of 11.

Now, how do we represent the number 4 in binary? Since we no longer have two-digit possibilities, we must use a three-digit number. The lowest three-digit number is 100. In the decimal system, this means “one hundred.” In the binary system, 100 means “four.”

Here is a chart showing decimal numbers up to 17 and how to represent them using the binary system.

Study this table to help you understand the binary sequence. Then try to continue the list to 32 (decimal), or 100000 (binary).

| Decimal | Binary |
|---------|--------|
| 0       | 0      |
| 1       | 1      |
| 2       | 10     |
| 3       | 11     |
| 4       | 100    |
| 5       | 101    |
| 6       | 110    |
| 7       | 111    |
| 8       | 1000   |
| 9       | 1001   |
| 10      | 1010   |
| 11      | 1011   |
| 12      | 1100   |
| 13      | 1101   |
| 14      | 1110   |
| 15      | 1111   |
| 16      | 10000  |
| 17      | 10001  |

## Changing Decimal to Binary

If you can divide by 2, you can convert decimal numbers to binary numbers. By repeatedly dividing a number, we can convert from decimal to binary. Remember that an even number divided by 2 will have a remainder of 0. An odd number divided by 2 will have a remainder of 1.

Let's convert the decimal number 8 to binary. You start by dividing 8 by 2, and then keep dividing the answer you get by 2.

|                                          |       |       |       |       |
|------------------------------------------|-------|-------|-------|-------|
| 8 divided by 2 = 4 with a remainder of 0 | _____ | _____ | _____ | _____ |
| 4 divided by 2 = 2 with a remainder of 0 | _____ | _____ | _____ | _____ |
| 2 divided by 2 = 1 with a remainder of 0 | _____ | _____ | _____ | _____ |
| 1 divided by 2 = 0 with a remainder of 1 | _____ | _____ | _____ | _____ |
|                                          | ↓     | ↓     | ↓     | ↓     |
|                                          | 1     | 0     | 0     | 0     |

We arrange the remainders like this:

This gives the binary number for 8: 1000. Check the decimal/binary chart shown earlier to make sure you are correct.

To practice again, convert 13 to a binary number.

|                                           |       |       |       |       |
|-------------------------------------------|-------|-------|-------|-------|
| 13 divided by 2 = 6 with a remainder of 1 | _____ | _____ | _____ | _____ |
| 6 divided by 2 = 3 with a remainder of 0  | _____ | _____ | _____ | _____ |
| 3 divided by 2 = 1 with a remainder of 1  | _____ | _____ | _____ | _____ |
| 1 divided by 2 = 0 with a remainder of 1  | _____ | _____ | _____ | _____ |
|                                           | ↓     | ↓     | ↓     | ↓     |
|                                           | 1     | 1     | 0     | 1     |

Arrange the remainders:

Check the decimal/binary chart and you will see that 1101 is the binary equivalent of 13.

## Changing Binary to Decimal

Changing numbers in the opposite direction is just as easy.

Let's convert the binary number 1001 to its decimal equivalent. In a way, we will do the opposite of what we just did; that is, instead of dividing by 2, we'll multiply by 2. First, write the binary number with the digits spread apart, like this:

1    0    1    1

Under the digit on the right, write the number 1. Multiply 1 by 2; the answer is 2. Write 2 under the next number. Multiply 2 by 2 (equals 4), and write 4 under the next number. Multiply 4 by 2 (equals 8) and write 8 under the next number:

1    0    1    1  
8    4    2    1

Now, add together the bottom numbers that appear under a 1.

In the example, 8, 2, and 1 are written under 1s, so  $8 + 2 + 1 = 11$ . Check the decimal/binary chart and you will see that 11 is the decimal number for 1011.

Here's another example. Convert the binary number 10110 to a decimal number:


1    0    1    1    0  
16   8    4    2    1

Adding the numbers under 1s, you get  $16 + 4 + 2 = 22$ .

Try some conversions on your own, checking the answers on the decimal/binary chart.
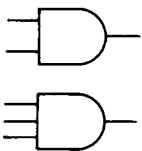
## Logic Circuits

Digital electronic devices consist of circuits called *logic gates*. A logic gate is a collection of transistors and resistors connected to perform a desired operation. The three basic types of logic gates are the *AND* gate, the *OR* gate, and the *inverter*, or *NOT*.



AND gates

### The AND Gate

The simplest AND gate has two inputs and one output. This circuit examines the input voltage levels and produces an appropriate output voltage level. Digital systems use the binary number system. Therefore, only two voltage levels are used. One voltage level stands for the number 0, and the other

stands for the number 1. A common arrangement is to let 0 volts represent the number 0 and to let +5 volts represent the number 1. An AND gate produces a 1 output only when all inputs are 1s. Or, it could be said that the output of an AND gate is true only if all inputs are true. So, for the arrangement explained above, the output of the AND gate is +5 volts (1) only when all inputs are +5 volts (1). If either input is 0 volts (0), the output will be 0 volts (0).

This gate is called an AND gate because the output is 1 only if input one *and* input two are both 1s. Some AND gates have more than two inputs. However, the operation performed is the same. For this reason, the AND gate can be thought of as an “all or nothing” decision circuit.

The illustration shows the logic symbol used in schematic diagrams for the AND gate. The inputs are shown on the straight side, the output on the curved side.

## The OR Gate

The OR gate, which has two or more inputs and a single output, also is a decision-making circuit. It produces a 1 (true) output when any one or all of its inputs are 1. That is, it produces a 1 output when input one *or* input two *or* both inputs are 1s. The only time the OR gate produces a 0 (false) output is when all inputs are 0. Think of it as an “any or all” decision circuit because if any or all of its inputs are 1, the output is 1.


## Inverter

The inverter has a single input and a single output terminal. If the input is 0, the output is 1. If the input is 1, the output is 0. That is, the inverter reverses, or inverts, the input.

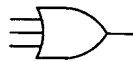
## Other Gates

Two other types of logic gates are used in digital electronics. One is the NAND gate. This circuit is composed of an AND gate and an inverter that are connected together. The output of the AND gate is applied to the input of the inverter as shown in the diagram above right. The NAND gate is shown as an AND gate with a bubble on the output to indicate that the result of the AND operation is inverted.

The output of the OR gate is applied to the input of the inverter as shown in the diagram above right. The NOR gate is shown as an OR gate with a bubble on the output to indicate that the result of the OR operation is inverted.




**OR gates**

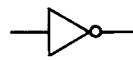

**Inverters**



**NAND gate**

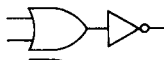

**NOR gate**

---

Logic gates generally are made in integrated circuit form. A single IC package may contain four NAND gates or six inverters.

---

## Digital Equipment

Connected in various ways, the basic logic gates can perform many different operations. Circuits have been devised to count, add, subtract, remember numbers, and solve complex problems. Large numbers of these circuits can be connected to form an array of useful electronic equipment. Sometimes, microprocessors perform many of the switching and timing functions of individual logic elements. The processors are programmed with instructions to perform a given task or tasks. Let's look at some popular digital devices.

### Computers

A computer can rapidly solve a wide range of problems and provide many other important functions. Computers are complex enough to be used to control spacecraft and airliners in flight. They are used in industry for calculating payrolls, for keeping records, word processing, and for inventory control, among other things. Besides “crunching numbers” for those functions, computers also can store and process data that are not mathematical in character. Such nonmathematical functions include ticket control by airlines, library record-keeping, and even translating languages.

In the 1950s, very few people had television sets. Now almost everyone does. The same thing has happened with the personal computer (PC) over the past 25 years or so. Once rare, now they are commonplace. Initially designed for individual use, PCs can be connected to form networks in a single office or all over the world.



**Laptop computer  
with cover removed**



Computers have essentially replaced the typewriter for writing and have many other uses, such as for sending faxes, communicating through electronic mail (email), and drawing, as well as for entertainment.

To use a computer, we must communicate with it. First, a programmer must write a *program*, or a set of instructions, that the computer's processor can understand. The program is designed to perform a needed task. The computer follows the program's instructions and performs the task. Most computer programs are extremely complex and are developed by several programmers at companies that specialize in developing these programs. Consumers usually buy these programs in the form of *software*. The computer and what it is connected with (such as printers) are the *hardware*.

The user, or operator, communicates with the computer through input devices such as a keyboard, a mouse, and a monitor, which can resemble a small TV set. The user enters information directly into the machine through the keyboard or a touch screen and interacts with application programs that usually have been stored on the PC's storage device, such as a hard disk (commonly called a *hard drive*). This is an inflexible platter or platters that are coated with material that allows the magnetic recording of data.



### Electronic Calculators

A calculator uses the same type of arithmetic circuits as a PC uses, but the method of entering data and displaying the answer is more simplified. The operations of early calculators were generally limited to a few mathematical functions, but newer ones can perform many complex functions.

### Digital Clocks and Watches

Digital clocks and watches are replacing their mechanical counterparts. In digital devices, an extremely accurate oscillator produces thousands of pulses each second. Electronic circuits count these pulses and convert them to a display of the time in hours, minutes, and seconds. Smart watches with extremely powerful microcontrollers and various types of communications can do this function and many more.



### Test Equipment and Other Devices

Digital techniques offer several advantages in electronic test equipment (see the chapter “Electronic Test Equipment” on page 75). Digital voltmeters generally are more accurate and easier to read than the meter-movement type of instrument.

Other test instruments include the frequency counter, oscilloscope, multimeter, cable checker, and clamp meter.

Several other types of digital equipment are becoming increasingly popular, especially in the fields of entertainment and communications. Digital techniques now allow for better TV reception, and digital techniques are used in electronic musical instruments, audio and video recording, transmitters, appliances, video games, and mobile phones.





# Audio

The field of audio deals with frequencies that are within the range of human hearing. Devices such as compact disc (CD) players, DVD (digital versatile disc) players, MP3 (high-quality sound files compressed into digital format) players, cassette recorders, stereos, receivers, public address systems, and electronic musical instruments are among audio equipment.

## What Is Audio?

When we strike middle C key on a piano, the sound we hear is caused by a vibrating wire. The wire vibrates about 260 times each second. This causes the molecules in the air to vibrate at the same rate, producing a mild shock wave that travels in all directions. When the wave reaches us, our eardrums vibrate at the same frequency. As a result, we hear a pleasing tone of the same frequency produced by the piano.

Middle C frequency is about 260 cycles per second, or 260 hertz (Hz). The piano's lowest note is about 27 Hz; the highest is higher than 4,000 Hz. Most people easily hear both extremes. A person with good ears can hear frequencies between 15 and




20,000 Hz. These extremes are considered the limits of the audio-frequency range. Audio equipment is used to produce, record, amplify, or reproduce frequencies in this range.

Most audio equipment falls in one of these categories:

- **“Hi-fi stereo” field.** A good CD player will faithfully reproduce any sound within the audio range. That is, it might have a frequency response from 15 to 20,000 Hz. Newer technology includes DVD-audio and SACD (super audio CD). DVD-audio has a frequency response up to 96,000 Hz, and SACD reaches 100,000 Hz.
- **The spoken word.** Public address systems and intercoms are in this category. The human voice covers a narrow frequency range (about 100 to 3,000 Hz), so the frequency response of such systems need not cover the entire audio range.
- **Musical instruments.** Electronic keyboards, synthesizers, and electric guitars are examples. These instruments produce a wide range of frequencies and can create many special effects.
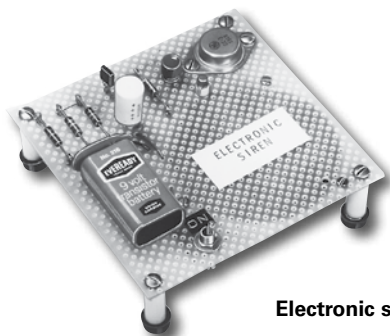
## Audio Project

Low-cost electronics kits are available that will satisfy requirement 4. However, you can build a simple audio device from scratch fairly easily, such as the electronic siren shown here. It produces a sound similar to a police siren. The frequency of the wail slowly increases as you hold down a push button, and when you release the button, the frequency of the wail slowly decreases.



**Electronic siren**


## Parts Needed

- ☐ Capacitor  $C_1$  50 microfarads, 12 volts, electrolytic
- ☐ Capacitor  $C_2$  0.018 microfarad, 25 volts or greater
- ☐ Transistor  $Q_1$  NPN, SK-3020 or equivalent
- ☐ Transistor  $Q_2$  PNP, SK-3009 or equivalent
- ☐ Resistor  $R_1$  27 k $\Omega$ , 1/2 watt, 10%
- ☐ Resistor  $R_2$  68 k $\Omega$ , 1/2 watt, 10%
- ☐ Resistor  $R_3$  56 k $\Omega$ , 1/2 watt, 10%
- ☐ Resistor  $R_4$  470 ohms, 1/2 watt, 10%
- ☐ Switch  $S_1$  Single-pole, push-button
- ☐ Switch  $S_2$  Single-pole, single-throw
- ☐ Speaker 3.2 to 8.0 ohms
- ☐ 9-volt battery
- ☐ Battery clip
- ☐ Perforated board
- ☐ Terminal posts (optional)
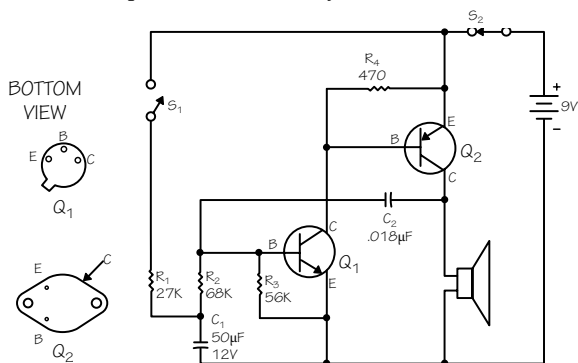
## Circuit Operation and Construction

The schematic diagram shown here is for the electronic siren. When  $S_1$  is closed, capacitor  $C_1$  begins to charge. As it does, it makes the base of  $Q_1$  more and more positive. This slowly turns on  $Q_1$ . Current through  $Q_1$  turns  $Q_2$  on;  $Q_1$  and  $Q_2$  form a direct-coupled amplifier.

Part of the output from  $Q_2$  is applied to the input of  $Q_1$  through capacitor  $C_2$ . This provides the regenerative (restoring) feedback that causes the circuit to oscillate (fluctuate). When switch  $S_1$  is opened,  $C_1$  discharges




Schematic diagram, electronic siren

through  $R_2$  and the base of  $Q_1$ . You can change the “wailing rate” of the siren by changing the values of  $R_1$  and  $C_1$ . An increase in the value of  $R_1$  or  $C_1$  lengthens the time period during which the frequency of oscillation increases.

Battery drain with switch  $S_1$  open is only about 400 microamperes. Therefore, power switch  $S_2$  is not necessary. But such a switch will add to battery life.

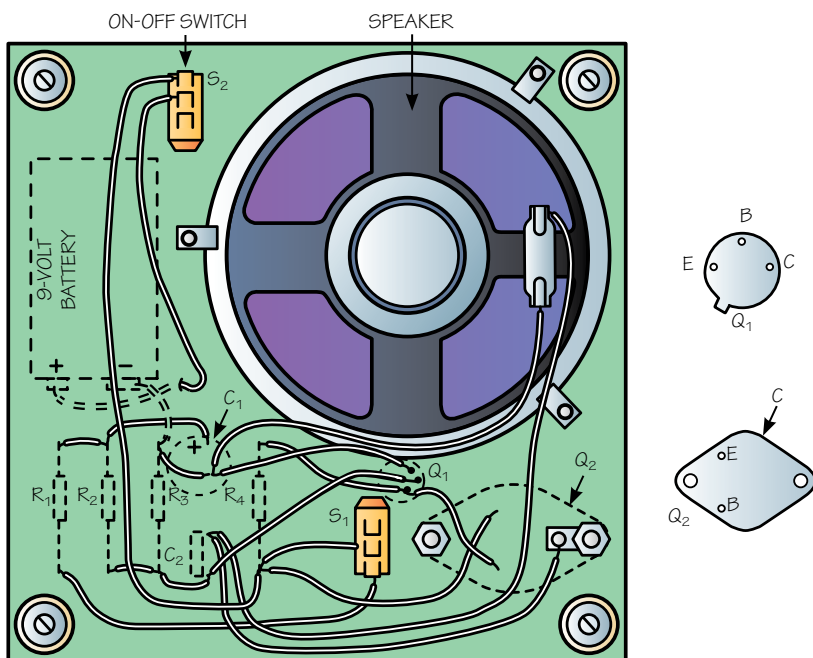You can get good results by building the circuit on a perforated board. All components except the speaker mount on top of the board. The illustration here shows all wiring connections as viewed from the bottom of the board. You can place the completed unit in a plastic box, or simply support the board on standoffs (legs) as shown.



**Wiring connections, bottom view**





# Electronic Test Equipment


Test equipment includes the instruments that are used to diagnose the operation of electronic circuits. The most popular types of test equipment are meters, oscilloscopes, and signal generators. You should use such equipment with someone who has experience using electronic test equipment.

## Meters

**Meter movement.** In electronics, meters are used to measure current, voltage, and resistance. Both analog and digital meters are popular, although digital meters continue to replace most analog meters. Digital meters are considered easier to use and to read.

In electronics, *analog* means a device or signal that is continuously varying in strength or quantity, such as a sound wave, rather than being based on separate units, such as used in the binary system of 0 and 1.

You have learned how basic digital technology works. How does an analog meter work? The heart of the analog meter is the meter movement. The meter movement consists of a coil of fine wire wound on a tight aluminum frame. The frame is suspended and free to rotate. The coil has leads attached so that current can be forced through it. The coil is suspended in the field of a permanent magnet. When current flows through the coil, a magnetic field develops around it. This field interacts with the field of the permanent magnet. The interaction of the two fields causes the coil assembly to rotate.

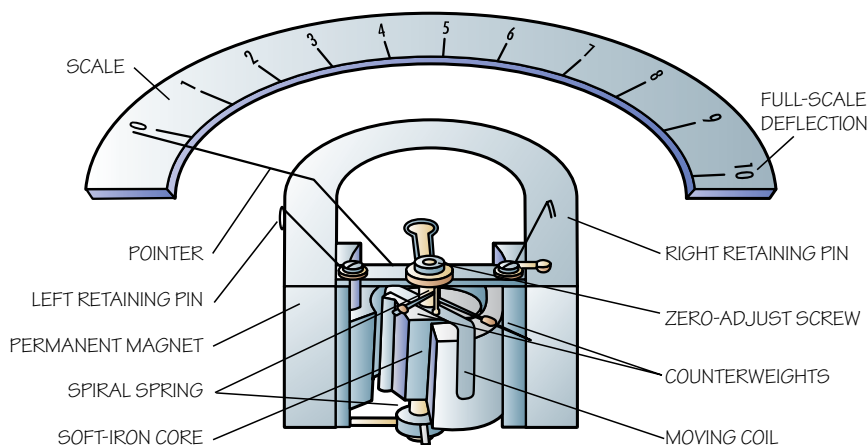


### Analog meter movement

The coil has a pointer attached to it, and as the coil rotates, it moves the pointer in front of a scale. The more current that flows through the coil, the farther the coil will rotate. This forces the pointer to move farther up the scale.

**Ammeter.** The ammeter is designed to measure current. The meter movement alone can be used as an ammeter. Normally, though, a range switch is added so that the meter can measure a wide range of current. The schematic for the ammeter shows a *shunt*. A shunt is a small value resistor that acts as a bypass. It detours some of the current around the meter movement. We can change the range of the ammeter by using a different value shunt across the meter movement.

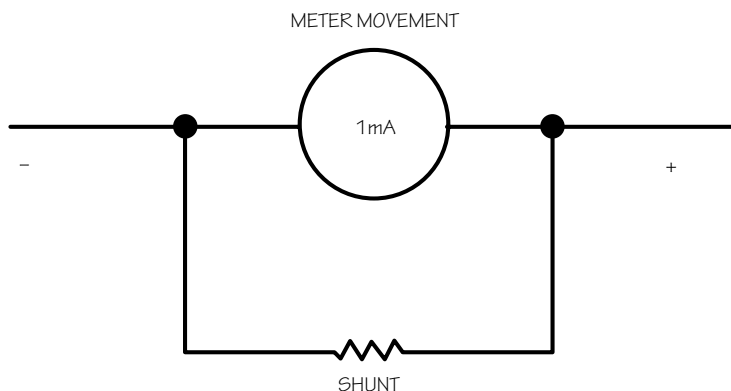An ammeter is delicate and easily damaged. It must be connected to the circuit so that the current to be measured flows through the meter. For this reason, the circuit being tested must be broken to insert the ammeter.



### Schematic of an ammeter

**Voltmeter.** The voltmeter is designed to measure voltage and uses the same type of meter movement as an ammeter. The voltmeter is connected across the voltage to be measured. To measure voltage between two points, touch the negative lead to the more negative point and the positive lead to the more positive point. The circuit under test need not be broken or interfered with in any way.


A low voltage can be applied directly to the meter movement. A higher voltage, however, might cause a high enough current to burn out the delicate coil. For this reason, a large-value resistor is connected in series with the meter movement. This resistor limits the amount of current flowing through the coil. Also, the meter should be set at the proper range. For instance, you shouldn't try to measure 100 volts with the meter set to the 1-volt range. Use the meter set on the high range if you are unsure of the voltage being measured.

The range of the voltmeter is changed by switching different values of resistors in series with the meter movement. On a given range, the voltage across the connected leads determines the current that flows through the meter. The meter scale can be marked off in volts.

---

When using a voltmeter, hold the meter leads *only* by the insulated portions to avoid getting an electrical shock.

---

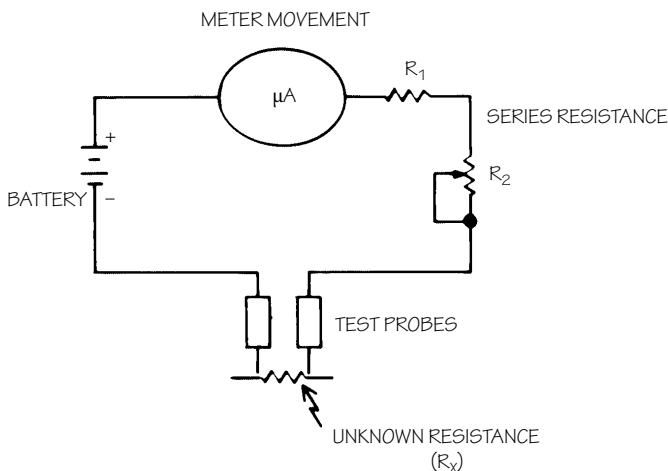


### Schematic of an ohmmeter

**Ohmmeter.** The ohmmeter measures resistance. It consists of a meter movement and a battery connected together. The ohmmeter should not be connected to a circuit that has power applied because the meter could be easily burned out if it is connected across a voltage.

The resistance to be measured is connected across the ohmmeter leads. The battery forces current through the resistance and through the meter movement. The amount of current depends on the resistance value under test. The range of the ohmmeter can be adjusted. For example, if the range is  $R \times 1$ , then a reading of 9 would measure 9 ohms. But if the range is set at  $R \times 1,000$ , then a 9 reading would mean 9,000 ohms (or 9 k $\Omega$ ).

**Multimeter.** The three types of meters we have just looked at use the same type of meter movement. For this reason, the ammeter, voltmeter, and ohmmeter can be combined in a single instrument called a multimeter, which displays the values of voltage, current, and resistance. A switch changes the meter movement from one function to the other. The multimeter is the most common piece of test equipment used in electronics work.

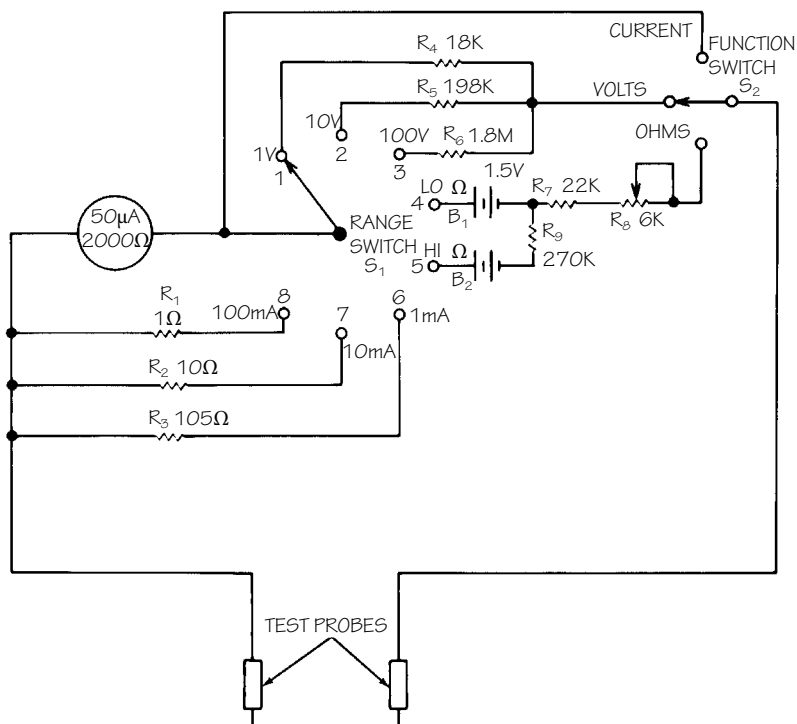

Schematic of a multimeter




These days, digital multimeters are the most popular.

## Oscilloscopes and Signal Generators


An *oscilloscope* looks something like a small TV, but the screen, or cathode-ray tube (CRT), shows voltage wave shapes. This lets you know how the voltage in a circuit changes over time.



Oscilloscope

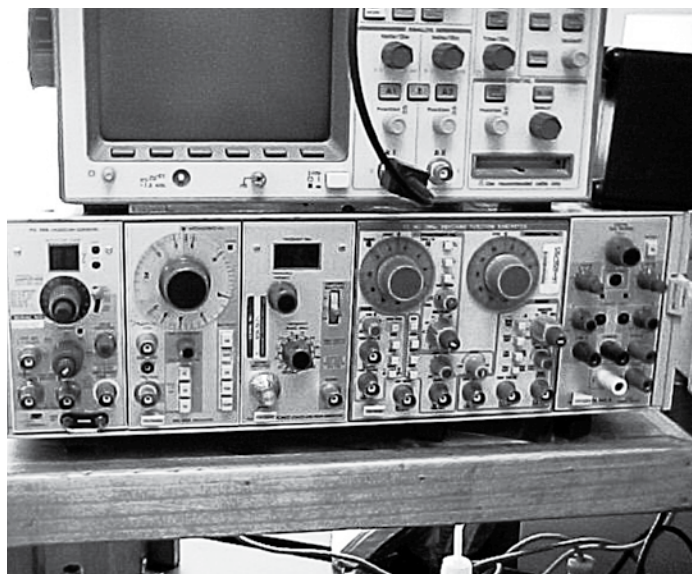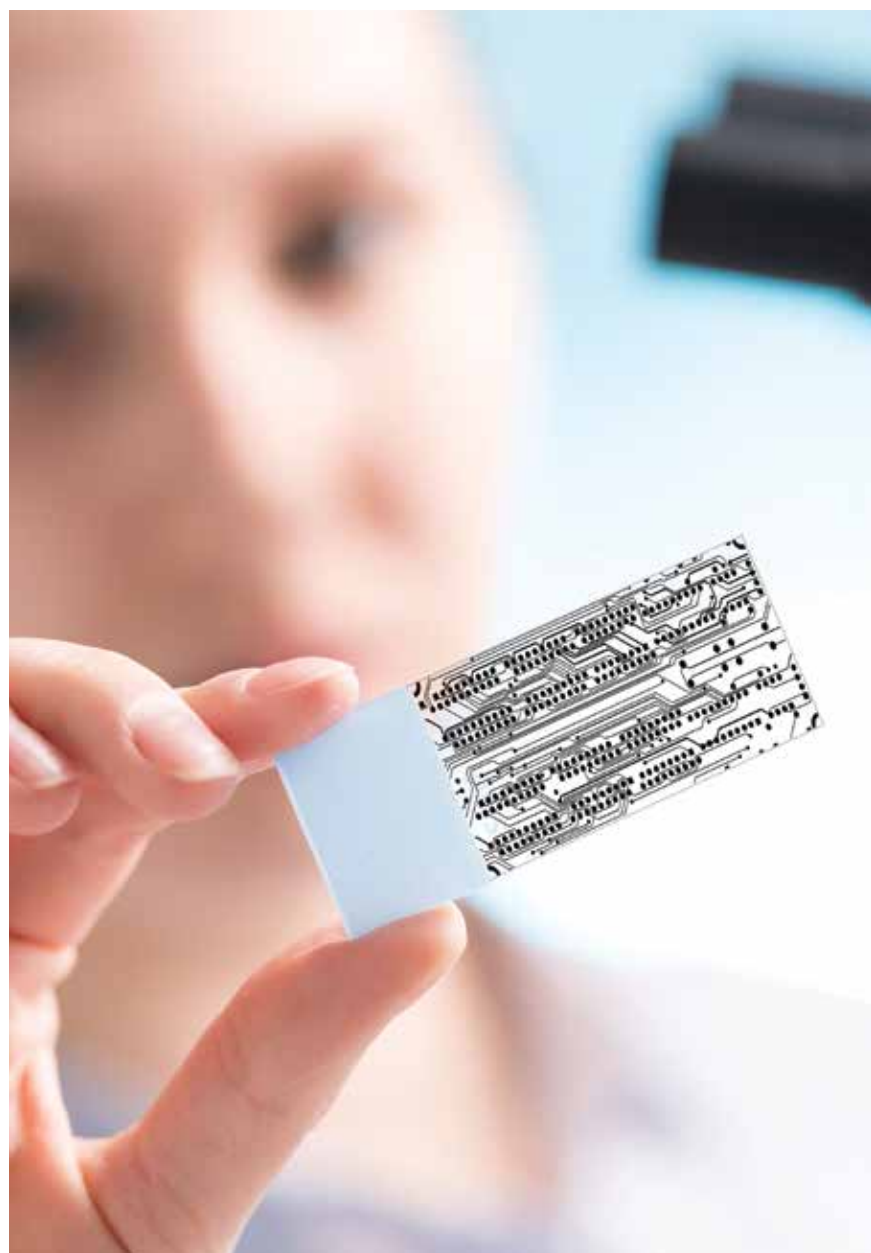**Signal generator**

Many different types of *signal generators* are used in electronics. The most common are used to align communications equipment and diagnose problems. These signal generators act as tiny replicas of transmitting stations. They allow service technicians to inject the proper type of signal at various points throughout the circuit. For this reason, the signal generator is a valuable troubleshooting aid. Many of today's signal generators can be hooked up to a PC, and the diagnosis can be seen on the computer monitor.



# Careers in Electronics

The electronics industry has several general areas with many types of careers available in each area. These areas include manufacturing, merchandising, operating, servicing or maintaining, and engineering electronic parts and equipment.

Training requirements vary in each area. Some positions require a college degree, while a degree from a vocational school is adequate for other careers. Some companies allow on-the-job training, but almost all require at least a high school diploma.

In *electronics manufacturing*, most positions are in factories. Occupations include assemblers, that is, the people who help build electronic equipment. A high school education is needed as well as mechanical aptitude.

*Merchandising*, or sales, is another field for those interested in electronics. Someone who has technical knowledge and enjoys talking with and meeting people could do well in electronics sales. Education can include a high school diploma or degrees from vocational schools and/or college.



Many types of electronics equipment are so specialized that they require trained *operators*. An operator might work with computers and computer network systems, cameras, satellite tracking devices, ship radios, or medical machines. In some cases, the operators must maintain and repair their own equipment. Education in a vocational school, a degree from a college or university, or training in the military usually is needed for these positions.

Because of the complexity of many electronic machines, *service and maintenance* people are always needed. Any electronic device can fail or malfunction from time to time, and people are needed to make quick and expert repairs.



*Technicians* can have a variety of positions. They might be required, among other things, to turn engineering ideas into hardware, to repair equipment, or to calibrate (adjust) test instruments. Most technicians have one or two years of technical training after high school. Some receive training in the military, and others go to a vocational school or junior college. Some receive on-the-job training or study at home by correspondence. Many occupations require continuous training so that technicians remain current with changing technology.

*Electronic engineers* usually have a bachelor's degree or higher in engineering. As with technicians, engineers must constantly update their education to keep abreast of new components and techniques. A highly trained electronics engineer might design electronic equipment or large electronic systems.



# Electronics Resources

## Scouting Literature

*Computers, Electricity, Inventing, Radio, and Robotics* merit badge pamphlets

With your parent or guardian's permission, visit Scouting America's official retail site, **scoutshop.org**, for a complete list of merit badge pamphlets and other helpful Scouting materials and supplies.

## Books

Bartholomew, Alan. *Electric Mischief: Battery-Powered Gadgets Kids Can Build*. Kids Can Press, 2002. Includes directions for an assortment of electronics.

Bonnet, Bob, and Dan Keen. *Science Fair Projects With Electricity & Electronics*. Goodwill Publishing House, 2014. Includes nearly 50 projects on electricity and electronics.

Bridgman, Roger. *Eyewitness: Electronics*. DK Publishing, 2000. Traces the history, discoveries, and devices of this fast-moving science.

Ceceri, Kathy. *Robotics: Discover the Science and Technology of the Future with 20 Projects*. Nomad Press, 2012.

Chirico, JoAnn. *Electronics*. VGM Career Horizons, 1996. This book explores career possibilities in electronics and electricity.

Engelbert, Phillis. *Technology in Action: Science Applied to Everyday Life*. Gale, 1998. A general look at technology and technical applications of scientific knowledge, with a section on computers and electronics.

Leon, George deLucenay. *Electronics Projects for Young Scientists*. Franklin Watts, 1991. Introduces the basic principles of electronics and includes project ideas such as a crystal radio, an intercom, and a pair of electronic dice.

Maxfield, Clive "Max." *Bebop to the Boolean Boogie: An Unconventional Guide to Electronics*, 3rd. ed. Newnes, 2009. This book covers the basics of electronics clearly, simply, and in an entertaining style.

Predko, Myke. *Digital Electronics Guidebook: With Projects!* McGraw-Hill, 2002. Introduces the nuts and bolts of digital electronics.

Rowh, Mark. *Opportunities in Electronics Careers*. McGraw-Hill, 2007. Check out the many electronics-related career opportunities featured in this book.

Slone, G. Randy. *TAB Electronics Guide to Understanding Electricity and Electronics*. 2nd ed. McGraw-Hill, 2000. A learn-as-you-go guide for readers of any electronics skill level.

## Magazines

### **Nuts & Volts**

430 Princland Court  
Corona, CA 92879  
Telephone: 951-371-8497  
nutsvolts.com

### **Popular Science**

popsci.com

## Organizations and Websites

### **American Microsemiconductor Inc.**

americanmicrosemi.com/tutorials

### **ePanorama.net**

epanorama.net

### **HowStuffWorks**

electronics.howstuffworks.com

### **101science.com**

101science.com/Radio.htm

## Electronics Parts and Suppliers

In many places, **Radio Shack** stores can be the best source for electronics parts. However, most Radio Shacks have reduced their parts inventories, which means you might have to look elsewhere to find all the parts you need for a project (or check out their website, [radioshack.com](http://radioshack.com)). Electronics parts and kits also can be ordered over

the internet or via mail or toll-free telephone from various suppliers.

Whenever you go online, be sure you have your parent or guardian's permission first.

### **All Electronics**

14928 Oxnard St.  
Van Nuys CA, 91411-2610  
Toll-free telephone: 818-904-0524  
allelectronics.com

### **Allied Electronics & Automation**

7151 Jack Newell Blvd. S.  
Fort Worth, TX 76118  
Toll-free telephone: 866-433-5722  
alliedelec.com

### **C&S Sales Inc.**

150 Carpenter Ave.  
Wheeling, IL 60090  
Toll-free telephone: 800-292-7711  
cs-sales.net

### **Carl's Electronics**

484 Lakepark Ave., Suite 59  
Oakland, CA 94610  
Toll-free telephone: 866-664-0627  
electronickits.com

### **Digi-Key Corporation**

701 Brooks Ave. S.  
Thief River Falls, MN 56701  
Toll-free telephone: 800-344-4539  
digikey.com

### **HobbyTron.com**

24700 Avenue Rockefeller  
Santa Clarita, CA 91355  
Telephone: 818-675-9000  
hobbytron.com

**Institute of Electrical and Electronics Engineers (IEEE)**

445 Hoes Lane  
Piscataway, NJ 08854-4141  
Telephone: 732-981-0060  
ieee.org

**Jameco Electronic**

1355 Shoreway Road  
Belmont, CA 94002  
Toll-free telephone: 800-831-4242  
jameco.com

**Mouser Electronics**

1000 N. Main St.  
Mansfield, TX 76063  
Toll-free telephone: 800-346-6873  
mouser.com

**Newark**

300 S. Riverside Plaza, Suite 2200  
Chicago, IL 60606  
Toll-free telephone: 800-463-9275  
newark.com

**SparkFun Electronics**

6333 Dry Creek Parkway  
Niwot, CO, 80503  
sparkfun.com

**Acknowledgments**

Scouting America thanks Norman McFadden for updating this version of the pamphlet. Thanks also to Mary Wiggins, director of educational initiatives for the Electronic Industries Foundation, for her assistance with this edition of the *Electronics* merit badge pamphlet. The EIF strives to create new ways to engage young people in the pursuit of science and technology, including electronics.

Scouting America is grateful to the men and women serving on the National Merit Badge Subcommittee

for the improvements made in updating this pamphlet.

**Photo and Illustration Credits**

University of Oklahoma, courtesy—page 89

SPARK Museum of Electrical Invention, sparkmuseum.org, courtesy—page 6 (*all foreground*)

Ultimate Symbols Inc., ©1996–2000—page 49 (*recycle symbol*)

Wikipedia.org, courtesy—page 41 (*resistors*)

All other photos and illustrations not mentioned above are the property of or are protected by Scouting America.

John McDearmon—all illustrations on pages 21–25, 29, 31–41, 55–56, 62–63, 71–72, and 76–79